

(v. 2/2015)

Rectifiers \rightarrow ac to dcInverters \rightarrow dc to ac

With rectifiers and inverters it's all about managing harmonics \rightarrow creating harmonics thanks to nonlinear nature of power electronics circuits
 \rightarrow Filtering out unwanted harmonics.

Good references:
 Dr Mohan's power electronics book


Dr Kreh's " "


Rectifiers

- Typically they can be single-phase or 3-phase
- The most simple topologies use diodes.
- The most common rectifier circuits convert ac-voltage to dc current

Let's start with the single-phase circuits.

Half wave:

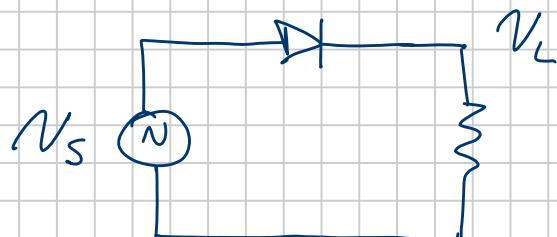


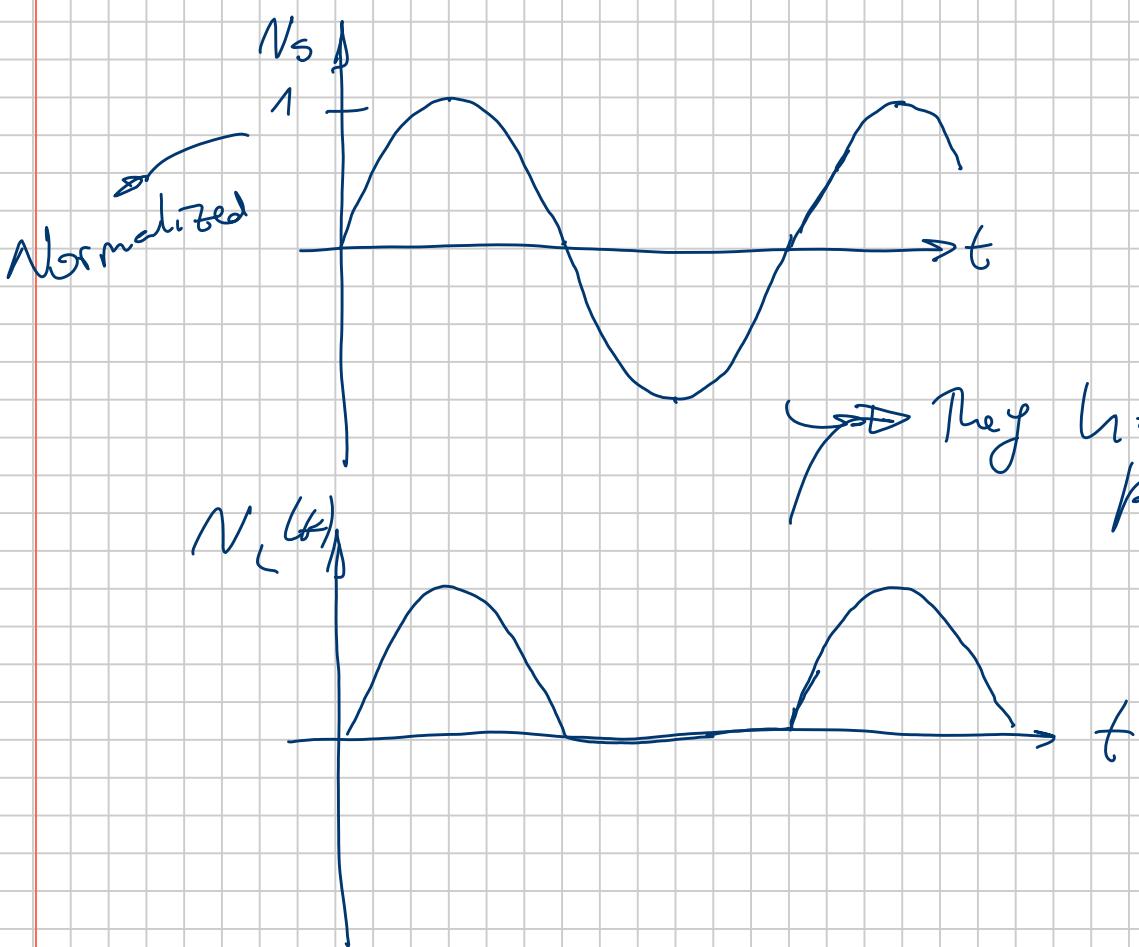


Since I want dc output, what's my dc component V_{dc} in $N_L(t)$?

$$V_{dc} = \frac{1}{T} \int_0^{T/2} \sin \frac{2\pi t}{T} dt = -\frac{1}{2\pi} \frac{1}{T} \left[\cos \frac{2\pi t}{T} \right]_0^{T/2} = -\frac{1}{2\pi} (\cos \pi - \cos 0) = \frac{1}{\pi}$$

let's see a full wave rectifier

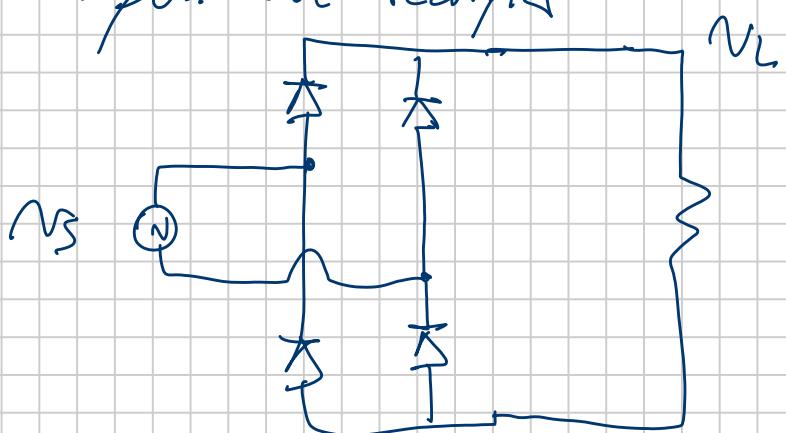

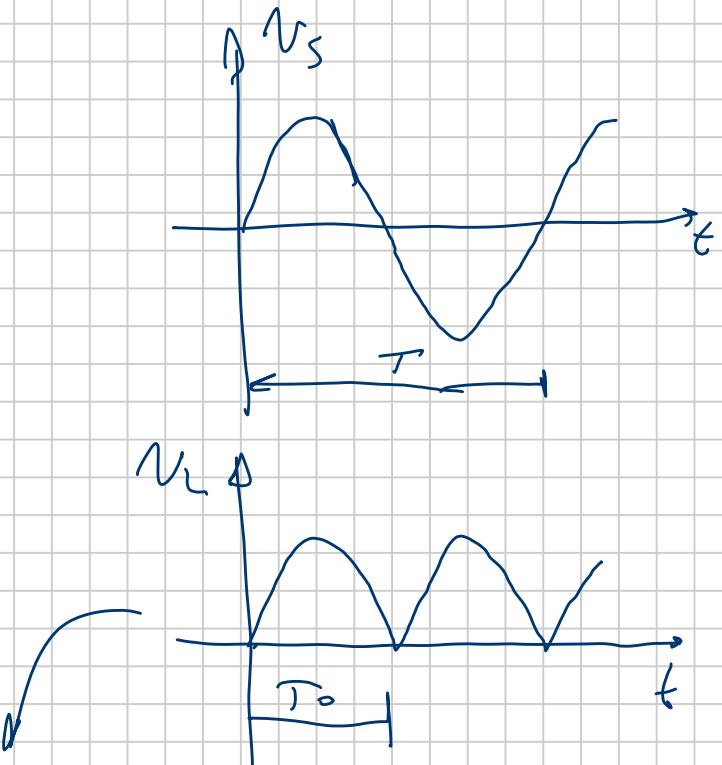

Doubles the input frequency

dc component:

$$V_{dc} = \frac{1}{T_0} \int_0^{T_0} \sin\left(\frac{2\pi}{T} t\right) dt = \frac{T}{2\pi T_0} \left(\cos\left(\frac{2\pi}{T} t\right) \right) \Big|_0^{T_0} = -\frac{1}{\pi} \left(\cos\left(\frac{2\pi}{T} T_0\right) - 1 \right) = \frac{2}{\pi}$$

So the dc component is double than in the previous case

What about the harmonic content.

Remember that $V_{rms}^2 = V_{dc}^2 + V_{harms}^2$

In the 1/2 bridge case

$$V_{rms}^2 = \frac{1}{T} \int_0^{T/2} \sin^2\left(\frac{2\pi}{T} t\right) dt = \frac{1}{T} \left(\frac{T}{2} - \frac{T}{4 \cdot 2\pi} \sin\left(\frac{4\pi}{T} t\right) \right) \Big|_0^{T/2} =$$

$$= \frac{1}{T} \left(\frac{T}{4} - 0 - \frac{T}{8\pi} \sin 2\pi + 0 \right) = \frac{1}{4}$$

$$\text{So } V_{h\text{ rms}}^2 = \frac{1}{4} - \left(\frac{1}{\pi}\right)^2 \approx 0.15$$

For the full bridge case:


$$\begin{aligned} V_{h\text{ rms}}^2 &= \frac{1}{T_0} \int_0^{T_0} \sin^2 \left(\frac{2\pi}{T} t \right) dt = \frac{1}{T_0} \left(\frac{t}{2} - \frac{T}{4\pi} \sin \frac{4\pi}{T} t \right) \Big|_0^{T_0} \\ &= \frac{1}{T_0} \left(\frac{T_0}{2} - 0 - \frac{T}{8\pi} \sin \left(\frac{4\pi T_0}{T} \right) - 0 \right) = \frac{1}{2} \end{aligned}$$

$$V_{h\text{ rms}}^2 = \frac{1}{2} - \left(\frac{2}{\pi}\right)^2 \approx 0.095$$


So in the full bridge not only there is a smallest harmonic content but it is at a double frequency. Hence, it is easier (but not easy) to filter than in the 1/2-bridge case.

How do we filter it? Well, if we want to keep the dc component only then we need a low-pass filter.

The simplest one is just one capacitor:

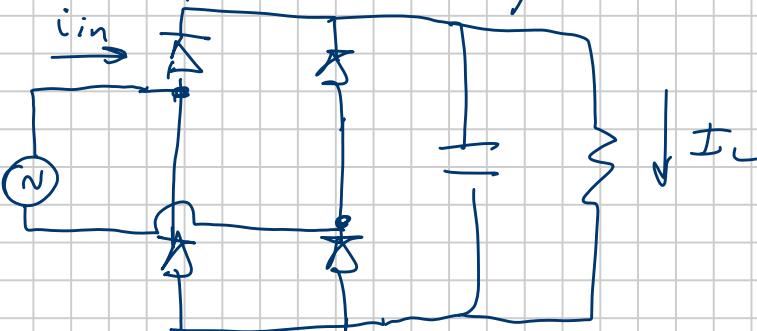

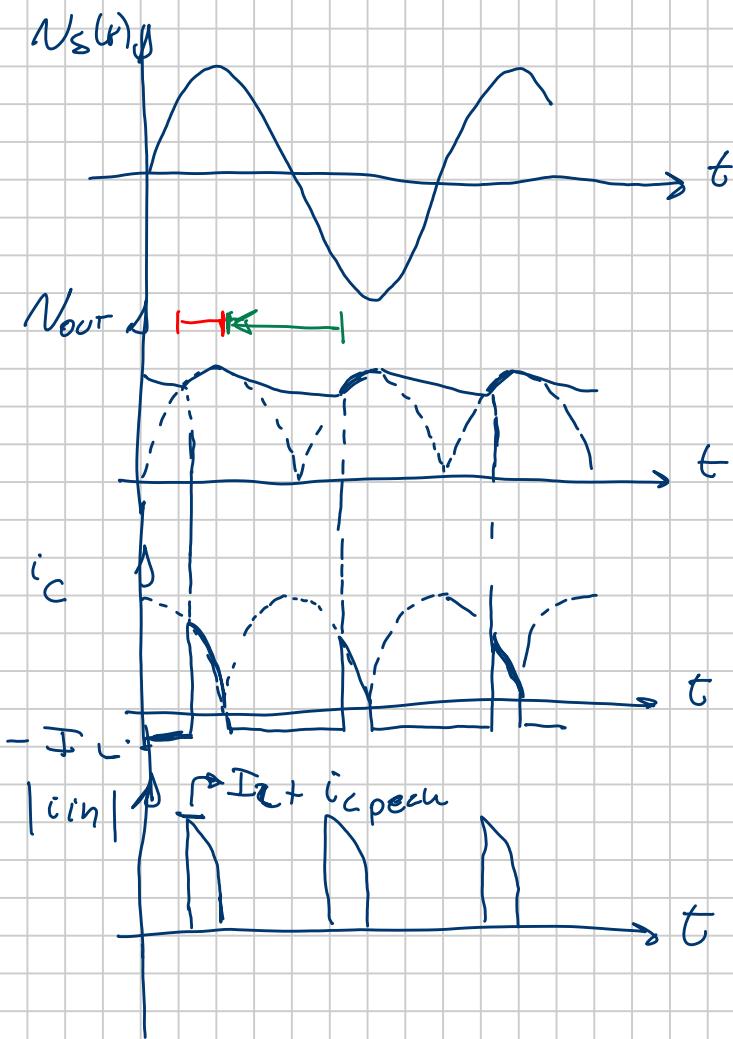But, we still need a "large" capacitor. Let's see the waveforms.



The capacitor needs to hold the load for a long time

↓
- capacitor discharges

- capacitor charges

$$i_{in} = I_L + i_C$$

$$i_C = C \frac{dV_C}{dt} = C \frac{d(\sin \omega t)}{dt}$$

$$i_C = |C \omega \cos \omega t|$$

What is the output voltage ripple?

Well, from

$$i_C = C \frac{dV_C}{dt}$$



$$I_C \approx C \frac{\Delta V_C}{\Delta t}$$

Hence,

$$\Delta V_c \approx \frac{I_L \Delta t}{C}$$

$$\therefore \Delta V_c \approx \frac{I_L (t_d - t_c)}{C}$$

If C is large enough $t_c \approx 0$ and $t_d \approx T/2$


\therefore

$$\Delta V_c \approx \frac{I_L T/2}{C}$$

$$T \Delta V_c \approx \frac{I_L}{2 f C}$$

Since f is the line frequency (at most a few hundred hertz in turbines), I usually need a "large" capacitor for "small" ripples

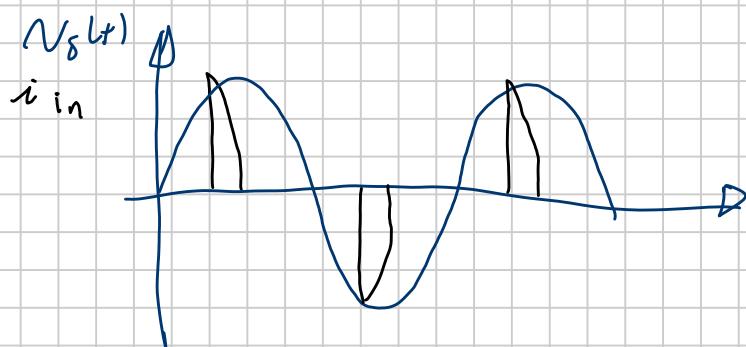The current and voltage at the source are:




What is the power factor as seen by the source

Remember

$$\text{PF} = \frac{P}{V_{\text{rms}} I_{\text{rms}}}$$

For $P = V_{rms} I_{rms} \cos \varphi$,

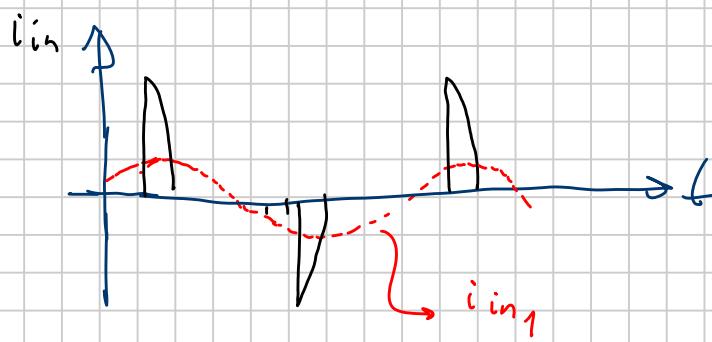


$$I_{in rms} = I_{m rms}^2 + I_{in h}^2$$

→ tends to be high when compared to I_m^2

because it is formed by pulses (higher content of higher harmonics)


So $\text{pf} = \frac{V_{rms} I_{rms} \cos \varphi}{V_{rms} (I_{in1 rms} + I_{m h})} < 1$

→ And in reality is quite low

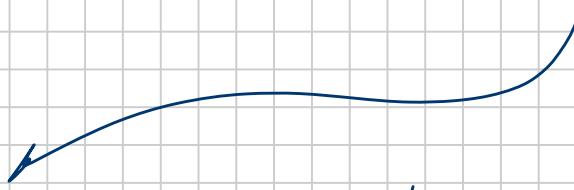

This is not good for the source

What can we do to improve this?

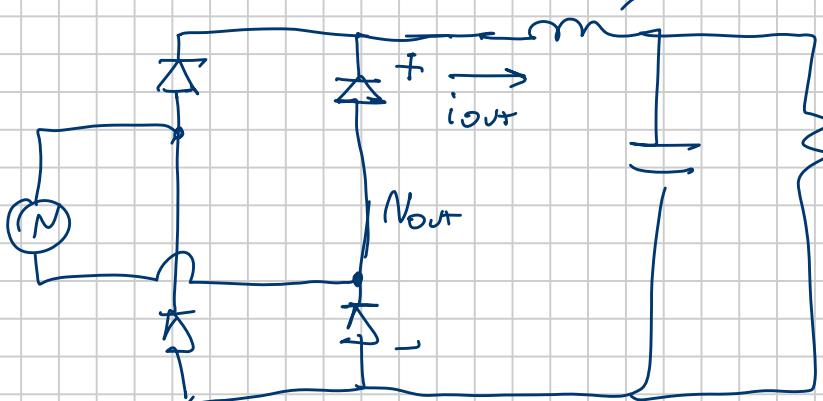


we can add
this inductor
in here.

it provides a
current interface


The inductor combined with the capacitor form a 2nd order low-pass filter. So the output is more constant with a smaller capacitor.

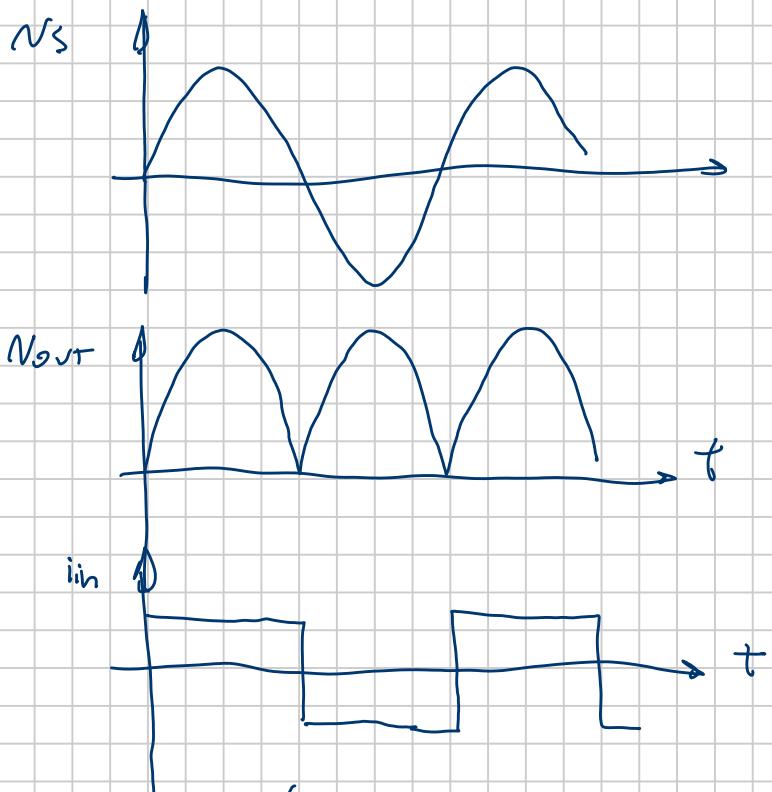With a "large" inductor current is approximately constant and equal to I_L . Then




Now i_{in} has a higher fundamental with respect to the harmonic content so the power factor is better but it can be still low.

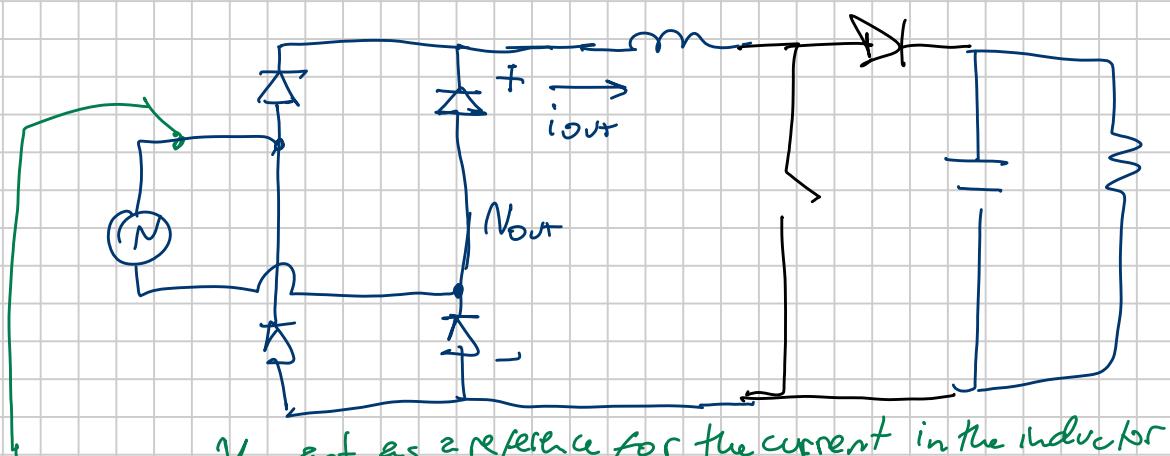One other solution to use a boost converter after the rectifier




V_s act as a reference for the current in the inductor

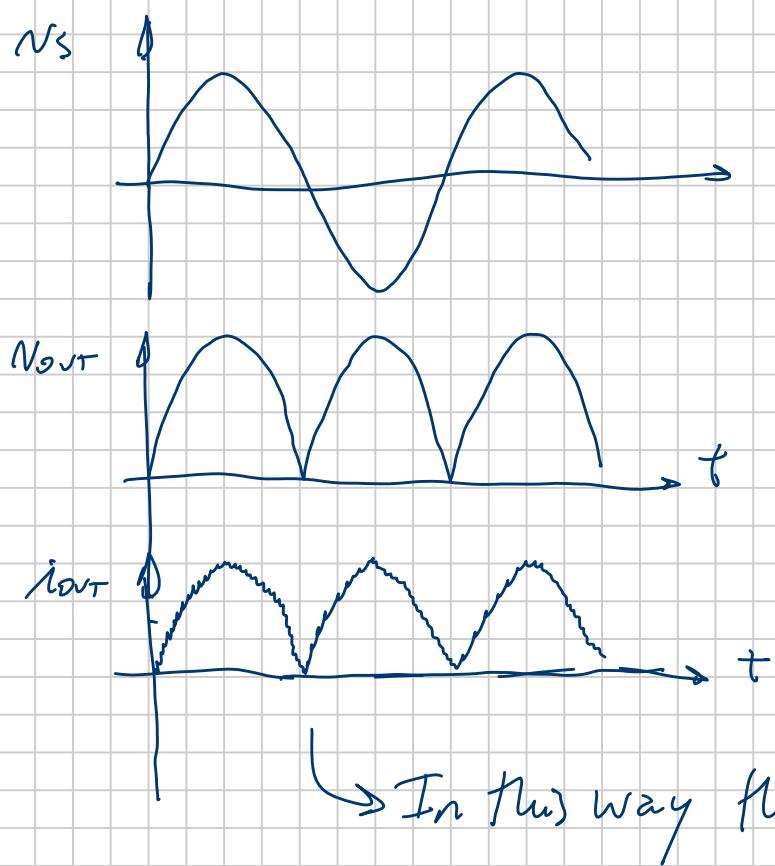The current in the inductor is controlled to follow the voltage in the source. The output capacitor takes care of the last filter stage.




In this way the $\text{pf} \approx 1$.

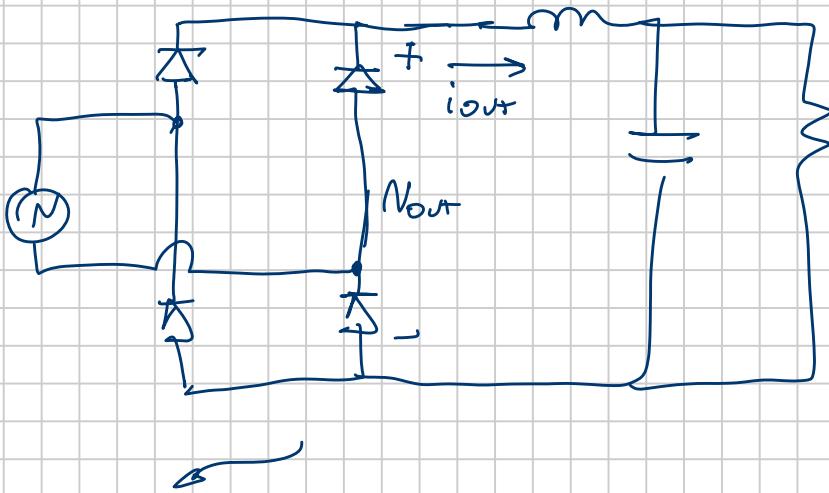
let's see some additional issues in rectifiers




I can draw it as:

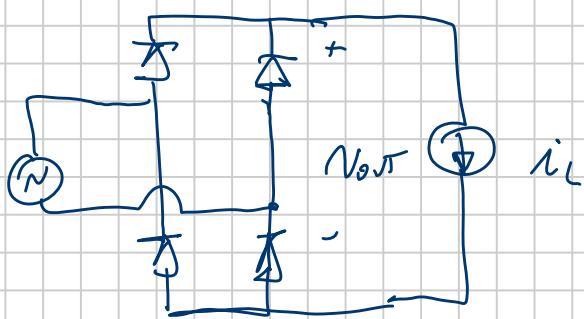

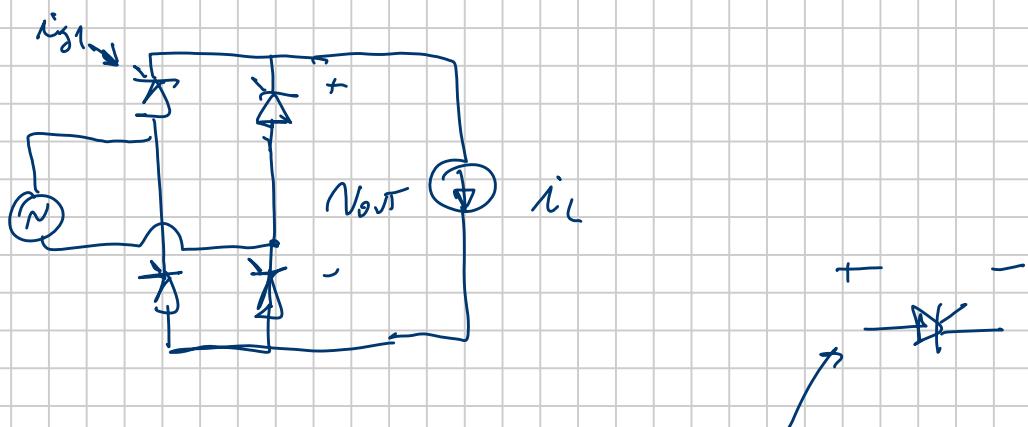One issue is that I cannot regulate my output (i.e., if V_s changes, V_{out} changes). One solution is to use SCRs instead of diodes:





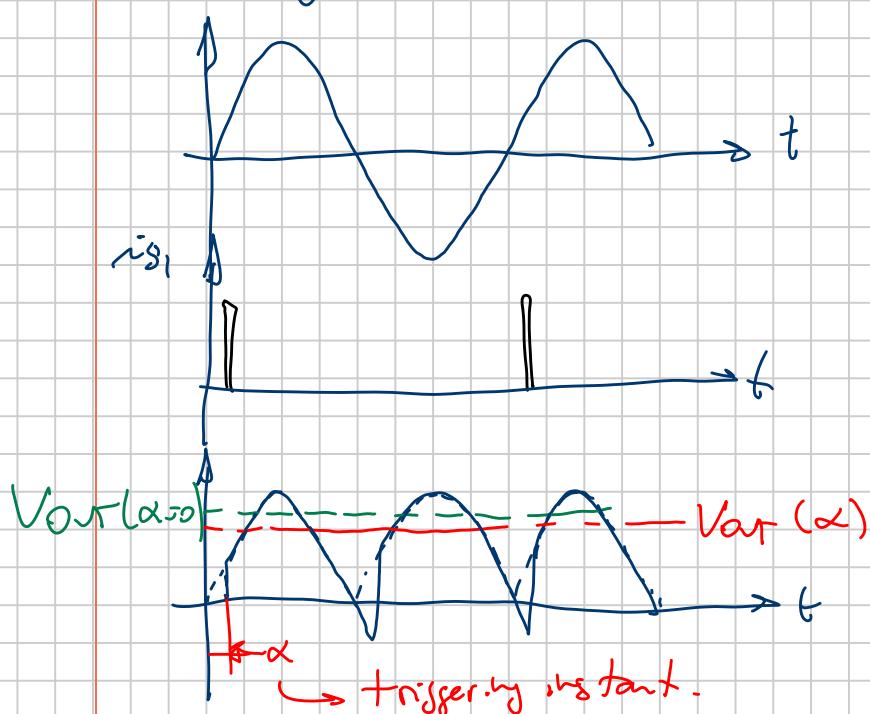An SCR conducts when it is forward biased and it has been triggered by injecting an adequate current pulse at the gate.





→ So I can now change V_{out} by changing α

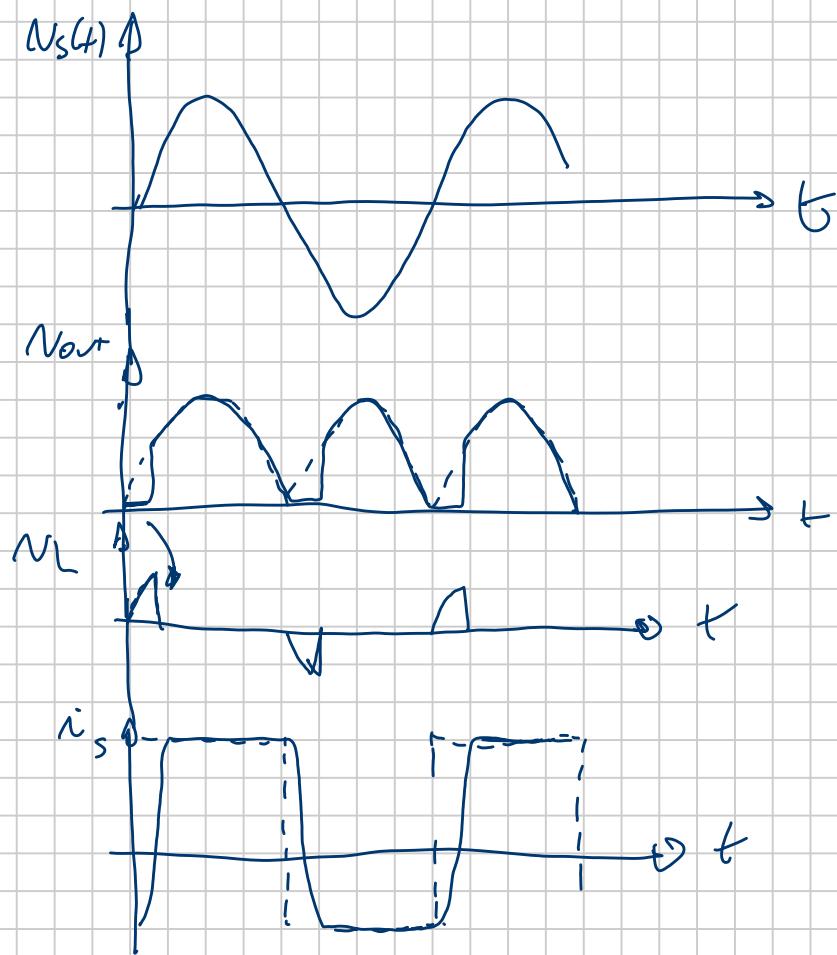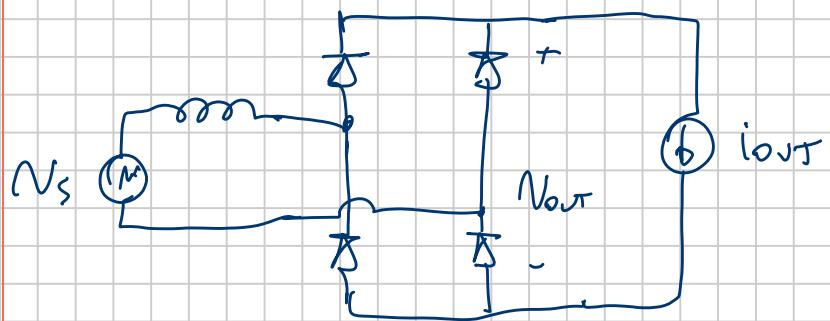Another issue is that most DG sources first require a rectifier (e.g. microturbine) have a current interface. So I actually have



So how do the curves look with a current input and voltage output?





↳ This is the most likely scenario

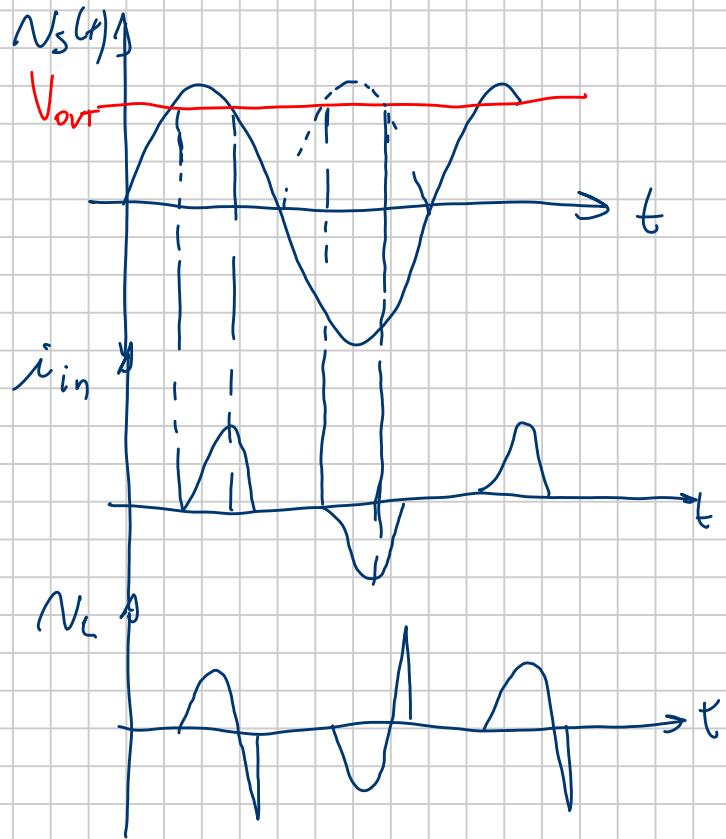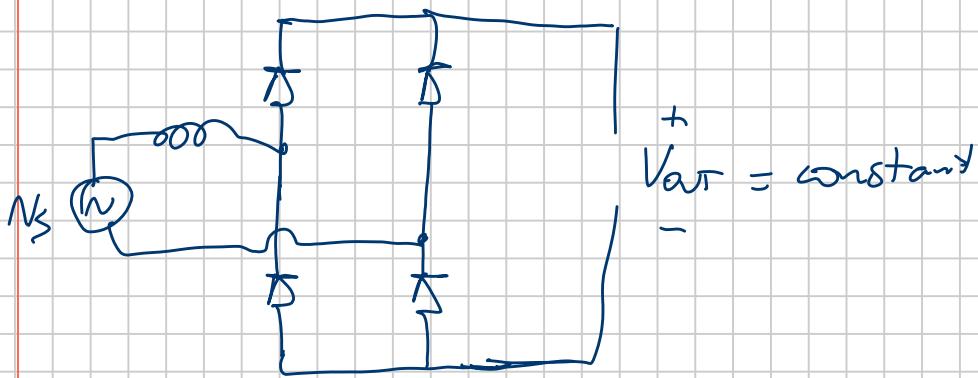

it yield a bad power factor


Needs to be compensated
e.g. dc link capacitor
and a boost converter

3-phase rectifier

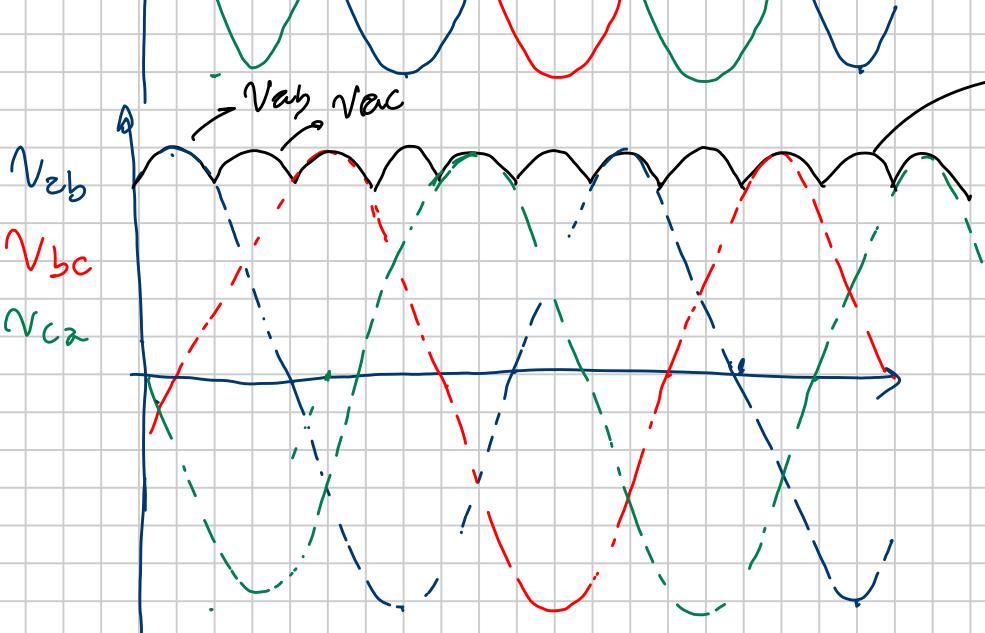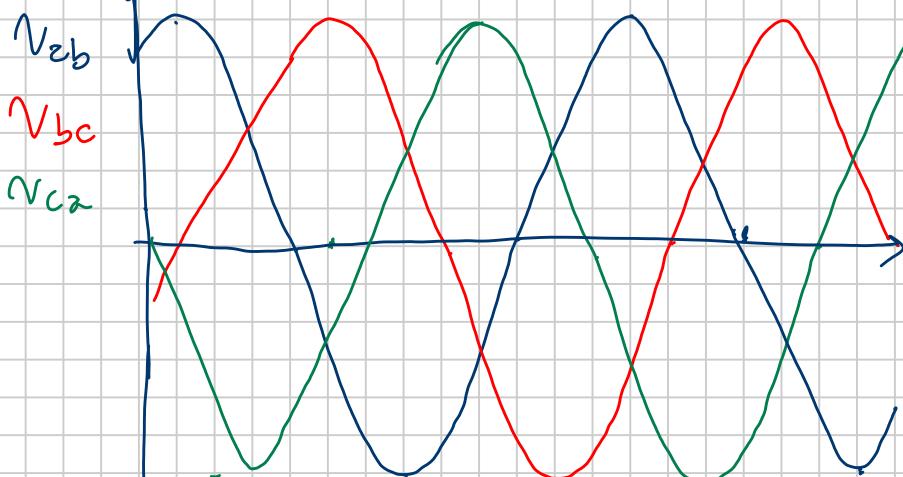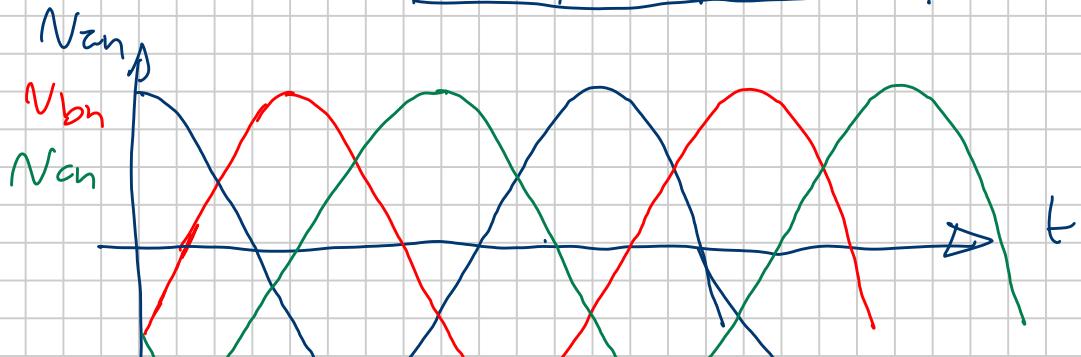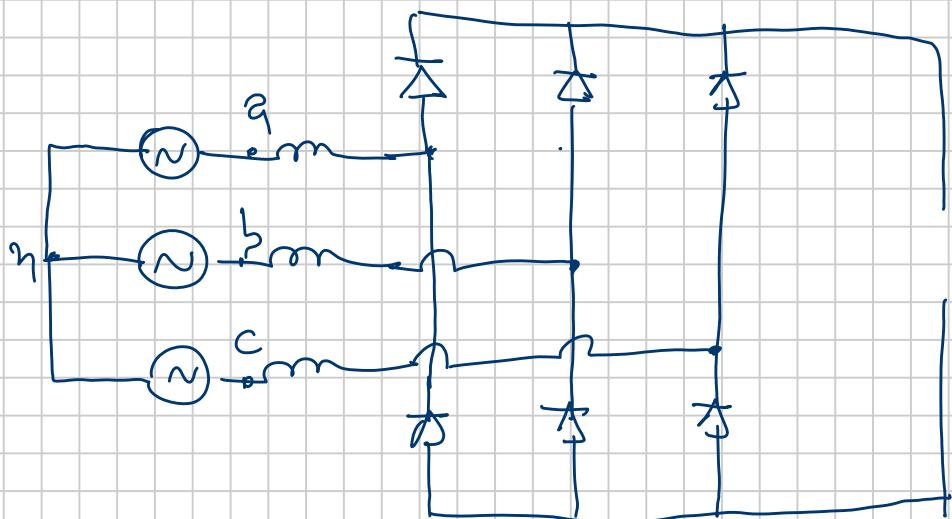


$V_{out} = \text{constant}$

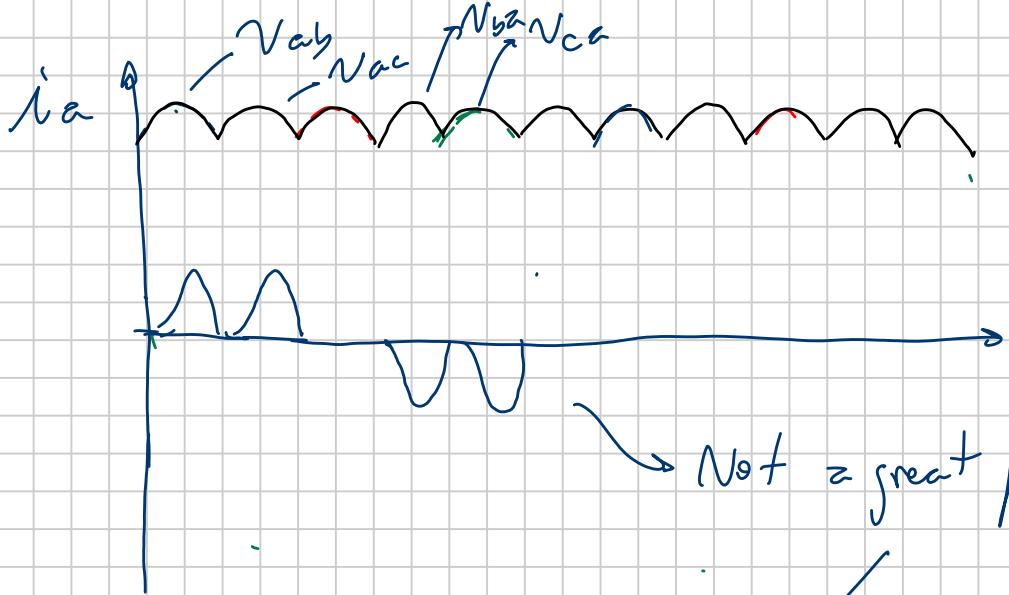$\rightarrow V_{out}$ unfiltered
 ↓
 its frequency
 is 6 times
 the line
 frequency
 (easier to
 filter harmonics)



it is also not as simple to compensate than in the single phase case

Generalized m-phase rectifiers

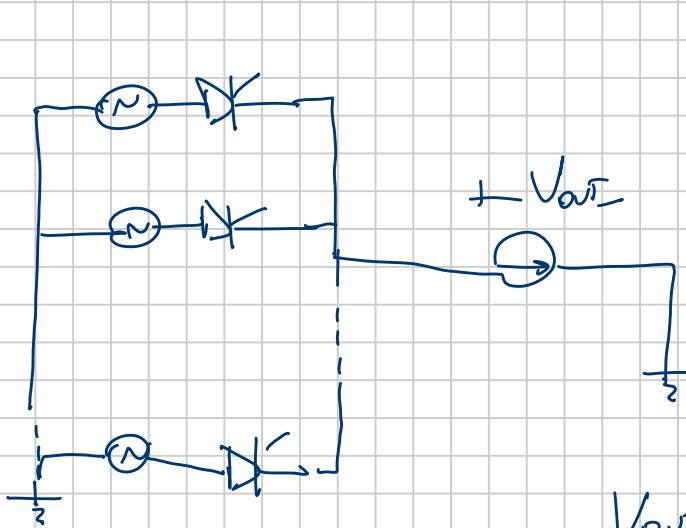


→ midpoint rectifier


$$V_{out} = \frac{m\sqrt{2}}{\pi} V_s \sin \left(\frac{\pi}{m} \right) \cos \alpha$$

for $m \geq 2$

Full bridge rectifier

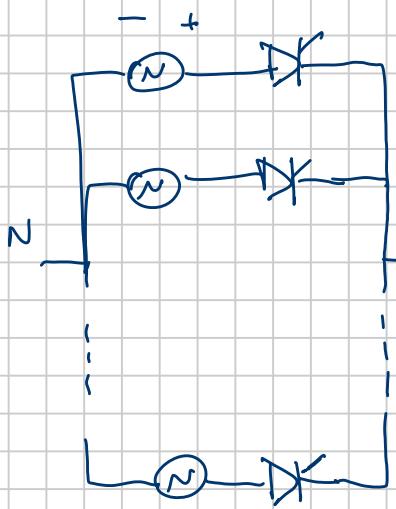

↑
mid point (m)

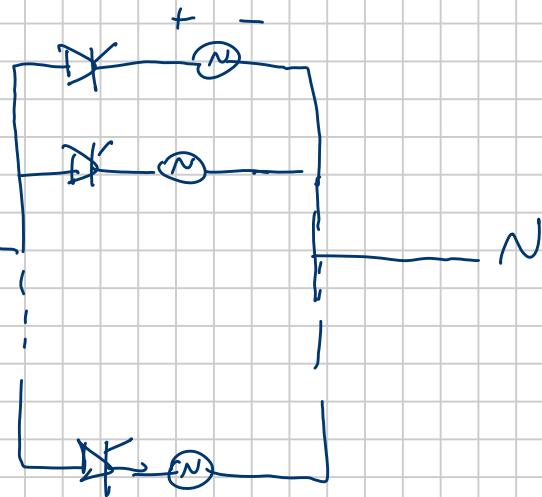

↑
Complementary (c)

$$V_{out} = \frac{\sqrt{2}}{\pi} V_{SL-L RMS} m \sin\left(\frac{\pi t}{m}\right) [\cos \alpha_n - \cos \alpha_c]$$

for $m \geq 2$


Special Case \rightarrow With diodes $\alpha_n = 0^\circ$, $\alpha_c = 180^\circ$ then

$$V_{out} = 2 \frac{\sqrt{2}}{\pi} V_{SL-L RMS} m \sin\left(\frac{\pi t}{m}\right)$$

Inverters

Understanding the switching function is essential for analyzing inverters behavior.

For $f(t)$ as:

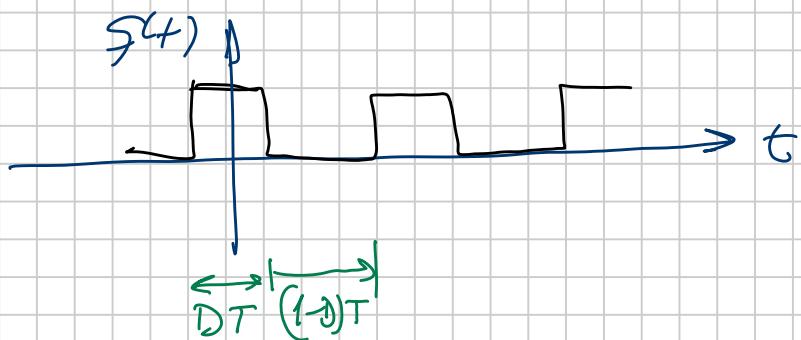


$$f(t) = D + \frac{1}{\pi} \sum_{n=1}^{\infty} \frac{\sin(n\pi D)}{n} \cos(\omega_0 t - n\phi_0)$$


↳ average value

$$|f(t)|_{avg} = \sqrt{D}$$

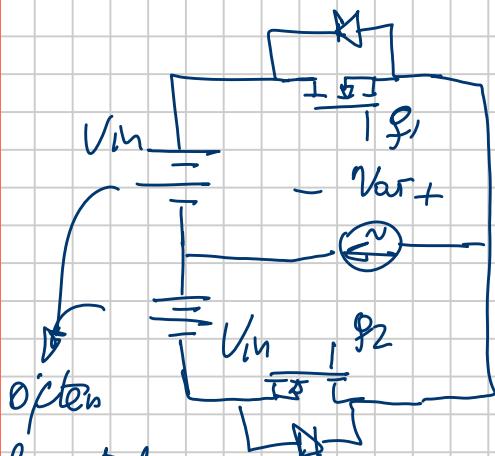Like we did with the rectifiers let's assume first a single-phase output half bridge inverter



Implemented

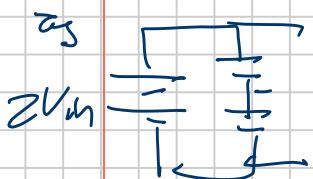

From LOVL $g_1 + g_2$ cannot be more than 1

From KCL $f_1 + f_2$ cannot be less than 1

∴ Hence, $f_1 + f_2 = 1$

$$\text{When } f_1 = 1, \text{ Vout} = V_h \quad \left\{ \begin{array}{l} \text{Vout} = g_1(+)V_h - g_2(+)V_h \\ \text{Vout} = (2g_1 - 1)V_h \end{array} \right.$$

$$\text{When } f_2 = 1, \text{ Vout} = -V_h$$

$$\text{Vout} = (2f_1 - 1)V_h$$

$$\langle \text{Vout} \rangle = \underbrace{(2D_1 - 1)V_h}_{\text{average}}$$

So if the load is inductive which requires $(N_L) = 0$,
then $\langle \text{Vout} \rangle = 0 \Rightarrow 2D_1 = 1$


$$D_1 = \frac{1}{2}$$

$$\text{and since } f_1 + f_2 = 1 \rightarrow D_1 + D_2 = 1$$

$$D_2 = D_1 = \frac{1}{2}$$

Since we want an ac output, then let's assume that
 $D_1 = D_2$ regardless of whether or not the load is
inductive.

Then ↴

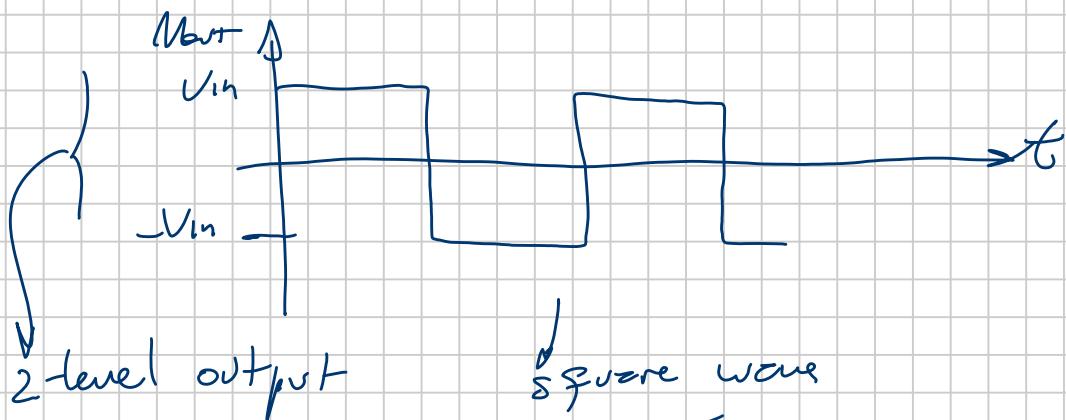

$$V_{out} = \frac{4V_{in}}{\pi} \sum_{n=1}^{\infty} \frac{\sin(n\pi/2)}{n} \cos(n\omega_{sw}t - n\phi)$$

it is obtained from $V_{out} = (2g_1 - 1)V_{in}$


$$\text{and } g_1(t) = \frac{1}{2} + \frac{2}{\pi} \sum_{n=1}^{\infty} \frac{\sin(\frac{1}{2}\pi n)}{n} \cos(n\omega t - n\phi_0)$$

$\underbrace{D}_{\frac{1}{2}}$

Usually we are mostly concerned with the fundamental



$$V_{out} = \frac{4V_{in}}{\pi}$$

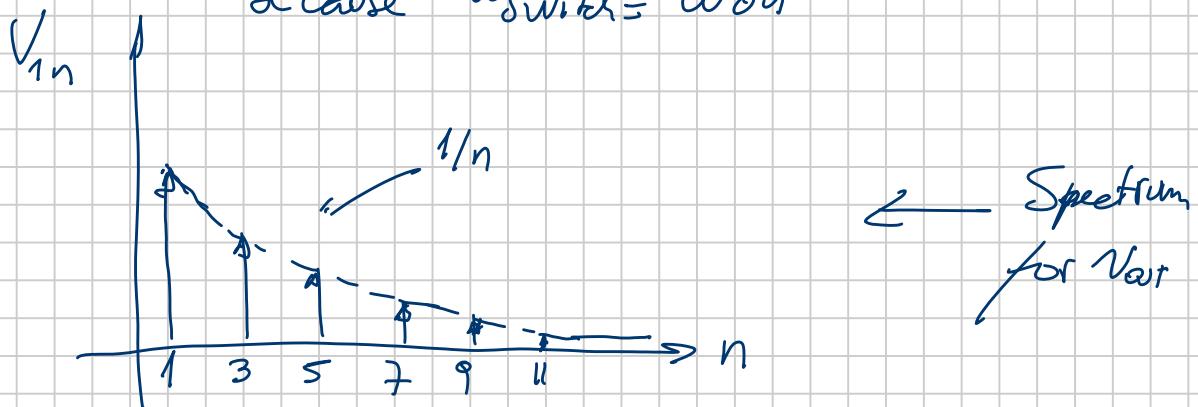- Issues:
- 1) Output is fixed \rightarrow No voltage regulation
 - 2) Harmonics too close to fundamental. And fundamental frequency is usually low because $\omega_{switch} = \omega_{out}$



How can we have output voltage regulation?

One solution is the following one:

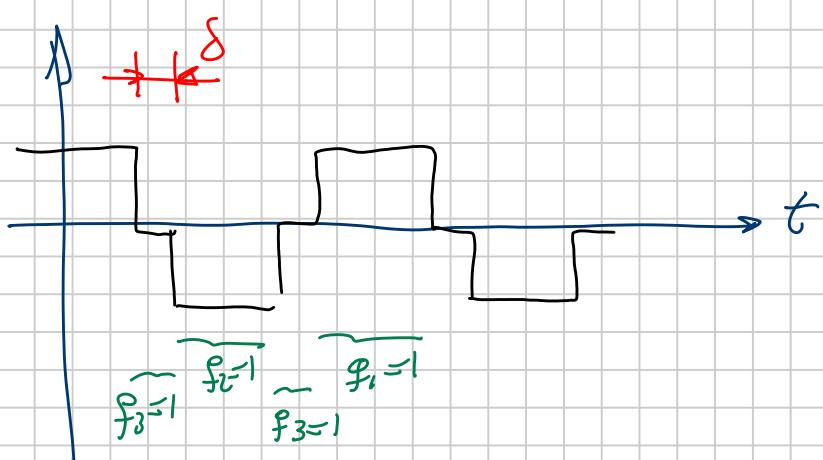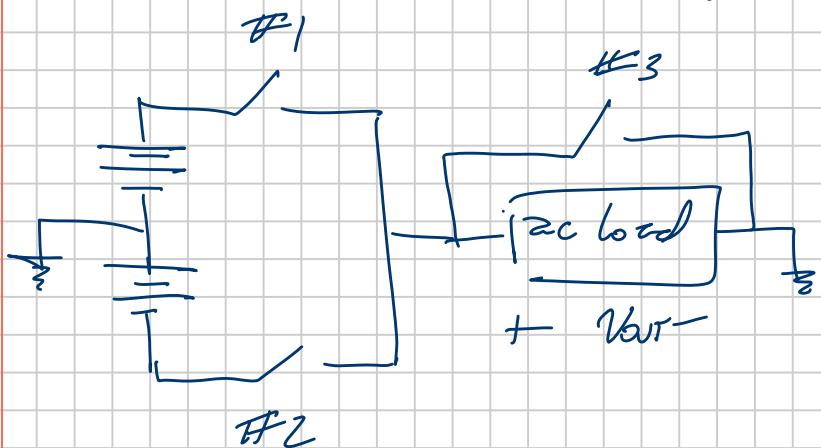


$$V_{out} = \frac{2V_{ib}}{\pi} \sum_{n=1}^{\infty} \frac{\sin(n\pi/2)}{n} \left[\cos(nwsut) + \cos(nwsut - \delta) \right]$$

The fundamental component is

$$V_{out_1} = \underbrace{\frac{4V_{ib}}{\pi} \cos \frac{\delta}{2} \cos \left(wsut - \frac{\delta}{2} \right)}_{V_{out_1}}$$

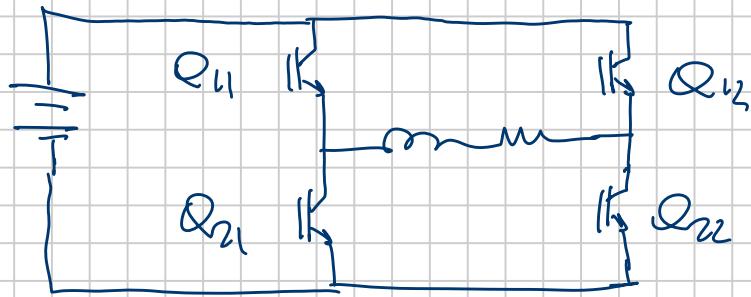I can achieve the same behavior with a full bridge inverter :



From KVL & KCL:


$$\left. \begin{array}{l} f_{11} + f_{21} = 1 \\ f_{12} + f_{22} = 1 \end{array} \right\}$$

If Q_{11} and Q_{21} or Q_{12} and Q_{22} are simultaneously on I have short-thru

$$\left. \begin{array}{l} Q_{11}, Q_{22} \text{ ON} \rightarrow V_{out} = V_m \\ Q_{12}, Q_{21} \text{ ON} \rightarrow V_{out} = -V_m \\ Q_{11}, Q_{12} \text{ ON} \rightarrow V_{out} = 0 \\ Q_{21}, Q_{22} \text{ ON} \rightarrow V_{out} = 0 \end{array} \right.$$

$$\left. \begin{array}{l} V_{out} = f_{11} V_m - f_{12} V_m = \\ = (f_{11} - f_{12}) V_m = \\ = (f_{11} + f_{22} - 1) V_m \end{array} \right.$$

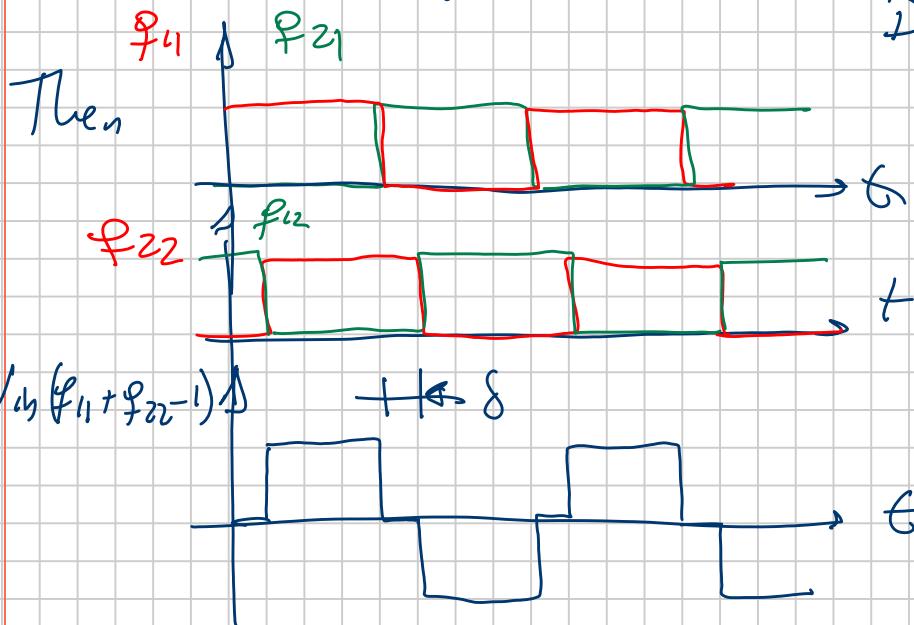
To avoid having dc we need $D_{11} = D_{21} = 1/2$
 $D_{12} = D_{22} = 1/2$



So I have addressed issue #1 above. But this approach does not address issue #2. Can I address both simultaneously? Yes, with pulse-width modulation (PWM).

PWM

Let's consider the inverter seen before

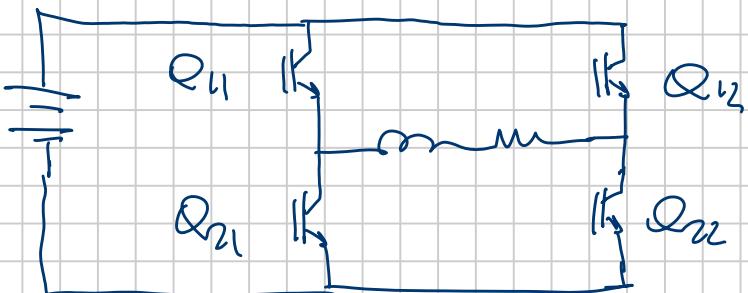

and let's operate it only with the following 2 states.

- { State1: Q_{11} ON and Q_{22} ON $\rightarrow V_{out} = V_{in}$
- State2: Q_{12} ON and Q_{21} ON $\rightarrow V_{out} = -V_{in}$

S_1 last for dT_S and S_2 lasts for $(1-d)T_S$ where d is the duty cycle for a given switching period and T_S is the switching period.

Although d stays fixed during each switching period it can change from switching period to switching period

My goal is to obtain an ac output in which the fundamental has a frequency of $\omega_b = 2\pi f_0 = \frac{2\pi}{T_0}$

So let's define k as

$$k = \frac{T_o}{T_s} \longrightarrow k \gg 1$$

Let's consider now one switching interval $\widehat{T_s}$.

During that particular switching interval d , is fixed and equals:

$$d = D | \widehat{T_s}$$

Then, the average output voltage for that switching interval $\widehat{T_s}$ is:

$$\langle V_{out} \rangle | \widehat{T_s} = D | \widehat{T_s} V_{th} + (1-D) | \widehat{T_s} (-V_{in}) = \\ = V_{th} (2D | \widehat{T_s} - 1)$$

This expression comes from $V_{out} = (g_{11} + g_{22} - 1) V_{in}$. If

$$g_{11} = g_{22} \text{ then}$$

$$\overbrace{\langle V_{out} \rangle = (2g_{11} - 1) V_{in}}^{\substack{\text{average} \quad \downarrow \\ \downarrow \text{average}}} \quad (1)$$

$$\langle V_{out} \rangle = (2D_{11} - 1) V_{in}$$

So from $\langle V_{out} \rangle | \widehat{T_s} = V_{th} (2D | \widehat{T_s} - 1)$ let's assume, as I said before, that the duty cycle changes' from switching cycle to switching cycle in the following particular way:

$$d(t) = \frac{1}{2} + \frac{1}{2} m(t)$$

where $m(t) = m \cos(\omega_0 t)$

modulator
Signal

modulation
index

desired
↑ fundamental
explosive

$$m \triangleq \frac{V_{\text{out}}}{V_{\text{ch}}}$$

where $m \leq 1 \quad \forall t \quad \text{so } |m(t)| \leq 1 \quad \text{and}$

$$|d(t)| \leq \frac{1}{2} \quad \forall t$$

so

$$d(t) = \frac{1}{2} + \frac{1}{2} m \cos(\omega_0 t)$$

and

$$\langle V_{\text{out}} \rangle(t) = V_{\text{ch}} m \cos(\omega_0 t)$$

The problem here is that I said

Although d stays fixed during each switching period it can change from switching period to switching period

And in the above equation d changes continuously with time. So the correct form is

$$D|_{T_s} = \frac{1}{2} + \frac{1}{2} m \cos(\omega_0 t(nT_s))$$

As $T_s \rightarrow 0$ ($f_{\text{sw}} \rightarrow \infty$) then $D|_{T_s} \rightarrow d(t)$

and $t(nT_s) \rightarrow t$.


So, how do I take $t(nT_s)$. In other words, how

do I sample the modulation signal?

There are 2 main approaches for sampling $m(t)$.

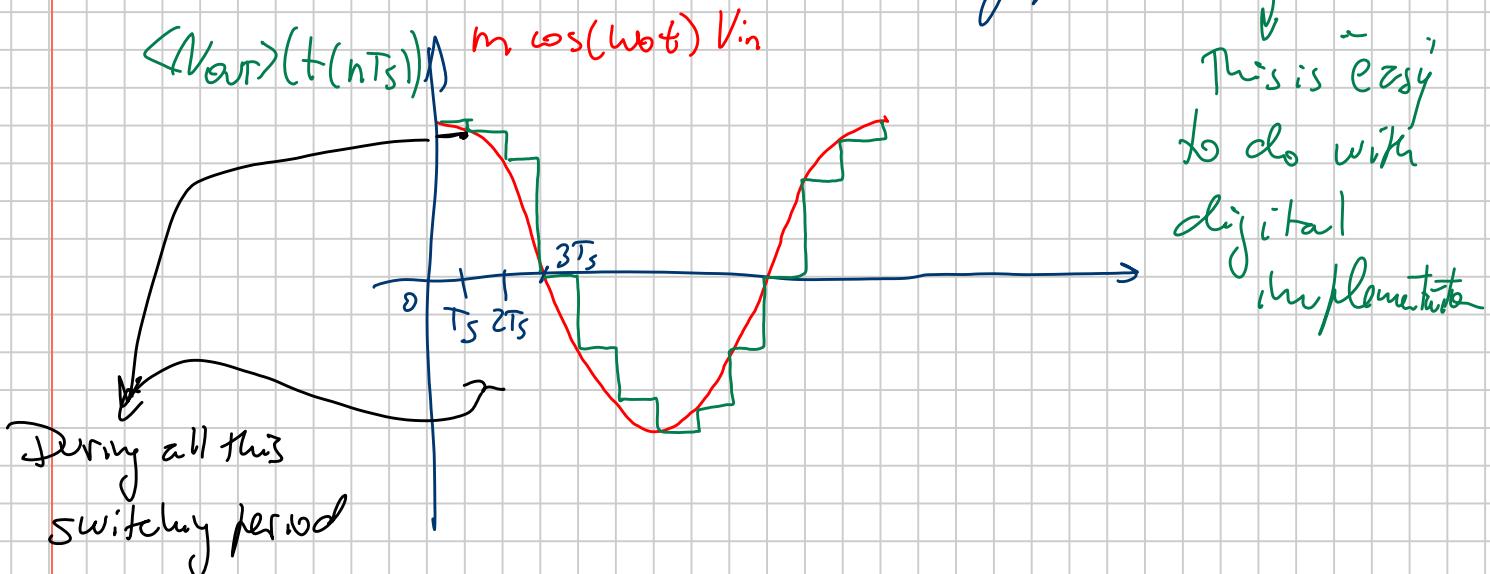
1) Uniform PWM (Upwm)

I sample every T_s seconds, usually at the start of each switching period.



$$D|_{T_s} = \frac{1}{2} + \frac{1}{2} m \cos(w_b T_s)$$

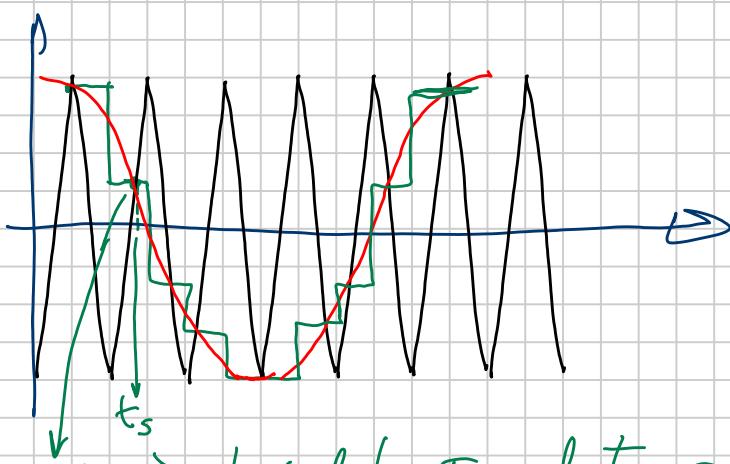
2) Natural PWM (NPWM) \rightarrow Sample is given by a triangle waveform




\rightarrow to find t_s I need to solve the transcendental equation $f_{t_s}(t_s) = m(t_s)$

This is difficult when it is implemented digitally

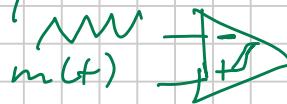
but it is easy when it is implemented
analogically



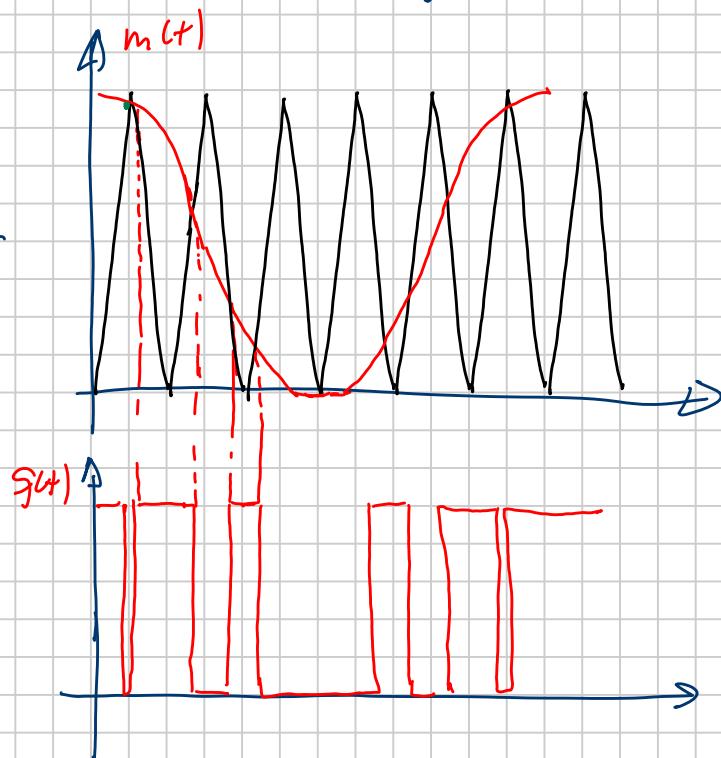$m(t)$ has, in fact, an offset of $1/2$ with respect to the red curve above. So $g(t)$ looks something like the following.




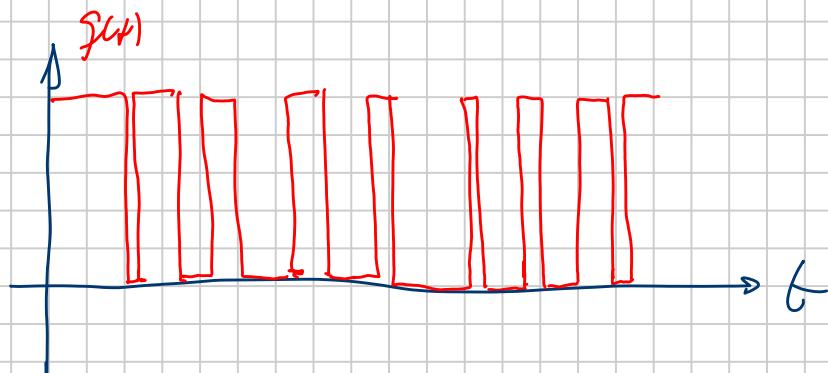Typically $T_s \ll T_0$ so $g(t)$ looks closer to the following



$$\text{And since } \text{Nbr} = (2g_{\text{in}}(t) - 1)V_{\text{in}}$$
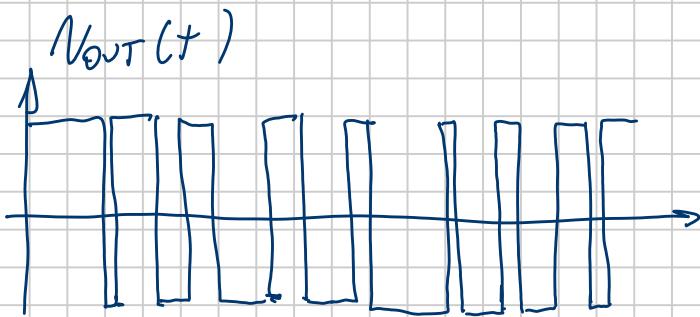
$$\text{if } d_{11}(t) = \frac{1}{2} + \frac{1}{2}m(t)$$



$$V_{out}(t) = \underbrace{\left(2 \frac{d}{T_S} - 1\right) V_{in} + \frac{4V_{in}}{T_S}}_{\langle V_{out} \rangle |_{T_S}(t)} \sum_{n=1}^{\infty} \frac{\sin(n\pi d/T_S)}{n} \cos(n\omega_{sw} t)$$

If $T_S \rightarrow 0$ then

$$V_{out}(t) = \left(2d_{11} - 1\right) V_{in} + \frac{4V_{in}}{T_S} \sum_{n=1}^{\infty} \frac{\sin(n\pi d_{11})}{n} \cos(n\omega_{sw} t)$$


$$V_{out}(t) = m(t) V_{in} + \frac{4V_{in}}{T_S} \sum_{n=1}^{\infty} \frac{\sin\left(n\pi\left(\frac{1}{2} + \frac{m(t)}{2}\right)\right)}{n} \cos(n\omega_{sw} t)$$


Fundamental


$$V_{out,1}(t) = m V_{in} \cos \omega_{sw} t$$


harmonic content

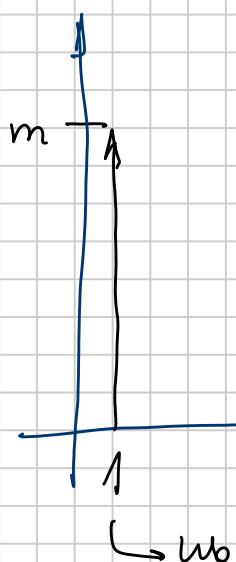
For T_S small (h large) both NPWM and UPWM yields the same spectrum for V_{out}



Spectrum for V_{out}

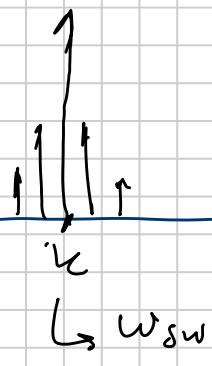

$\hookrightarrow \omega_{sw}$

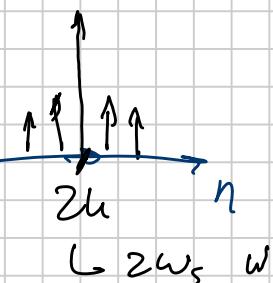


$\hookrightarrow 2\omega_0 \quad w$


In reality \rightarrow NPWN \rightarrow it is more difficult to implement
but doesn't have harmonics around the fundamental (ω_0)

\rightarrow UPW \rightarrow it's easier to implement but for low h it yields harmonics around ω_0

How do I filter the unwanted harmonics?

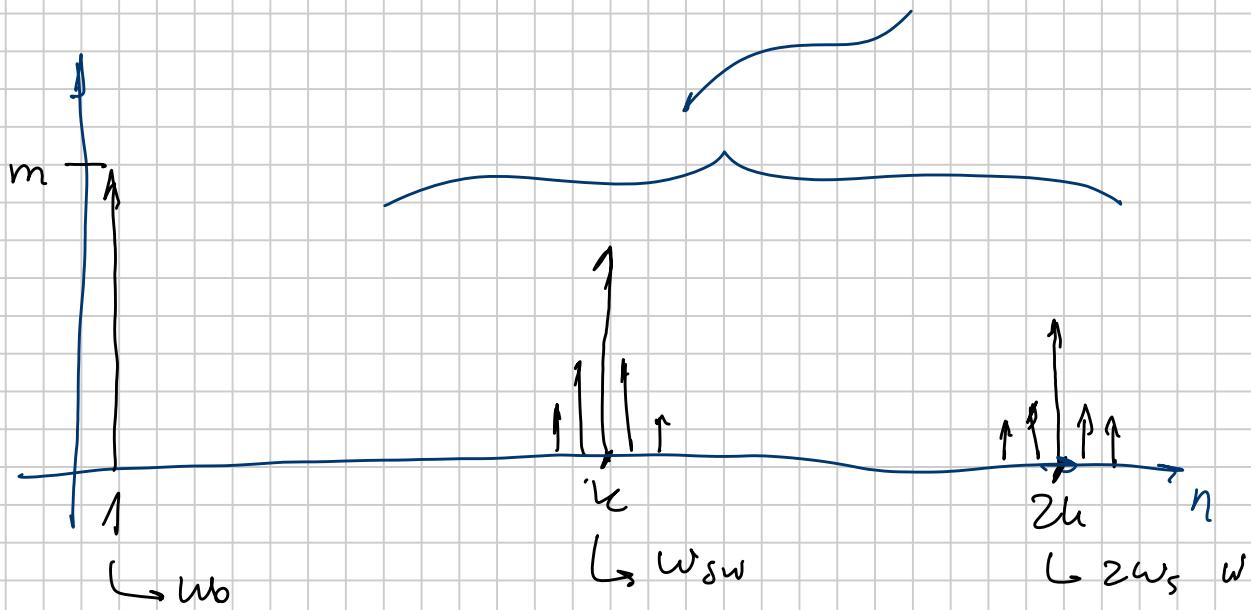


Answer: I use a low-pass filter:

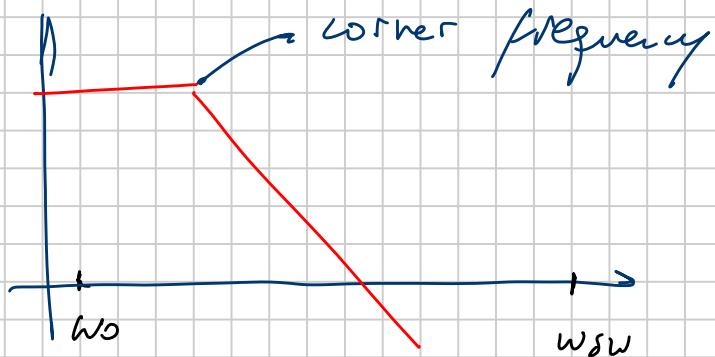


The advantage is that w_{sw} is away from w_0 , so I can reduce the size of my filter components by choosing a higher corner frequency

So the filter looks something like this.

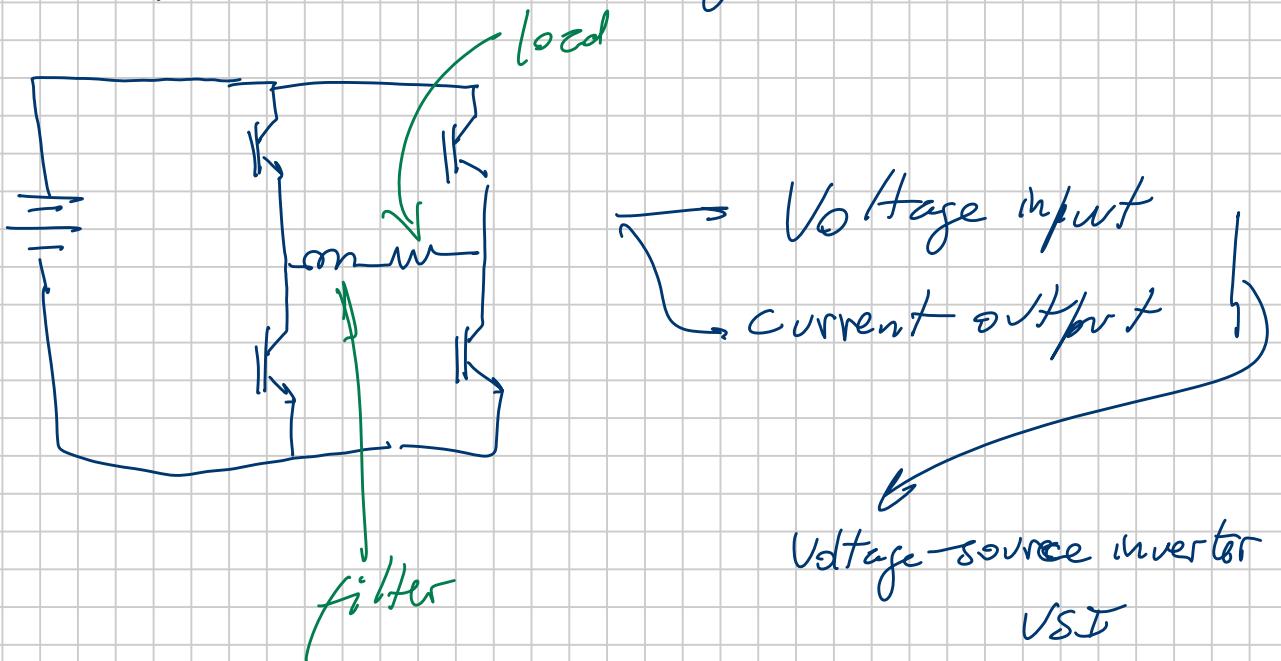

3-phase VSI:

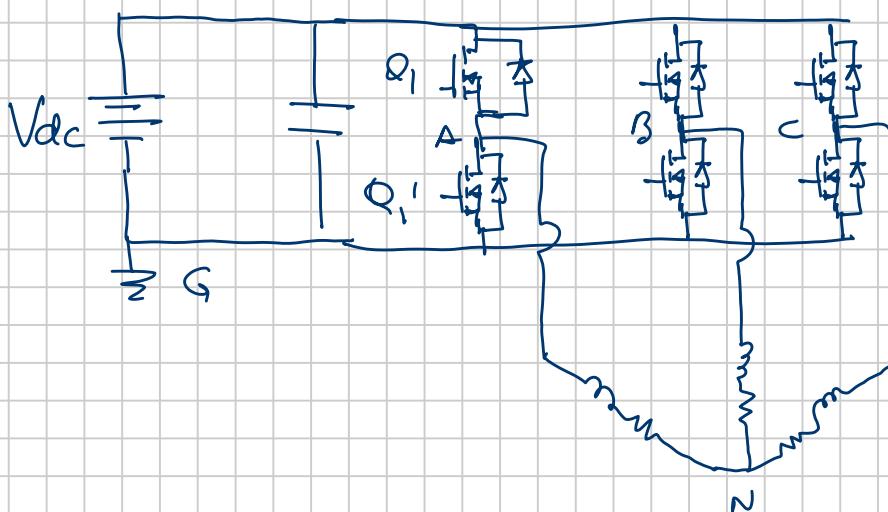

If Q_i and Q_{i'} are simultaneously on I have short-through
I need to add standby time

Possible voltages $V_{Aq}, V_{Bq}, V_{Cq} = \begin{cases} V_{dc} \\ 0 \end{cases}$

$$V_{AB}, V_{BC}, V_{CA} = \begin{cases} +V_{dc} \\ -V_{dc} \\ 0 \end{cases}$$

$$V_{AN}, V_{BN}, V_{CN} = \begin{cases} 2/3 V_{dc} \\ +1/3 V_{dc} \\ -1/3 V_{dc} \\ 2/3 V_{dc} \end{cases}$$

$$V_{AS} = \begin{cases} V_{dc} & \text{with } Q_1 = \text{on} \\ 0 & \text{with } Q_1 = \text{off} \end{cases}$$

$$V_{AS \text{ fund}}(t) = f_{11}(t) V_{dc} = \left(\frac{1}{2} + \frac{1}{2} m_a(t) \right) V_{dc}$$

↳ fundamental

In 3 phase systems: $m_a(t) = m \cos \omega_0 t$

$$m_b(t) = m \cos(\omega_0 t - \frac{2\pi}{3})$$

$$m_c(t) = m \cos(\omega_0 t + \frac{2\pi}{3})$$

$$V_{AB \text{ fund}} = V_{A \text{ fund}} - V_{B \text{ fund}} = \left\{ \frac{1}{2} m_a(t) - m_b(t) \right\} V_{dc} =$$

\uparrow
line voltage

$$= \left\{ \frac{1}{2} m \left[\cos \omega_0 t - \cos \left(\omega_0 t - \frac{2\pi}{3} \right) \right] \right\} \frac{V_{dc}}{\sqrt{3}}$$

$$= \frac{1}{2} m V_{dc} \sqrt{3} \cos \left(\omega_0 t + \frac{\pi}{6} \right)$$

$$V_{AB \text{ fund peak}} = \frac{\sqrt{3}}{2} m V_{dc} \quad \Rightarrow \quad m = \frac{V_{AB \text{ fund peak}}}{\sqrt{3} \frac{V_{dc}}{2}}$$

$$m = \frac{V_{AB \text{ fund peak}}}{\sqrt{3} \frac{V_{dc}}{2}} = \frac{-\sqrt{2} V_{AB \text{ fund rms}}}{\sqrt{3} \frac{V_{dc}}{2}} = \frac{\sqrt{2} V_{AB \text{ fund rms}}}{\frac{V_{dc}}{2}}$$


$$m = \frac{V_{AB \text{ fund peak}}}{\frac{V_{dc}}{2}}$$

→ half the gain
than a 1-phase
converter

Still we have a VSI \Rightarrow Voltage input, current output

Other topologies are:

- Current source interface (CSI)

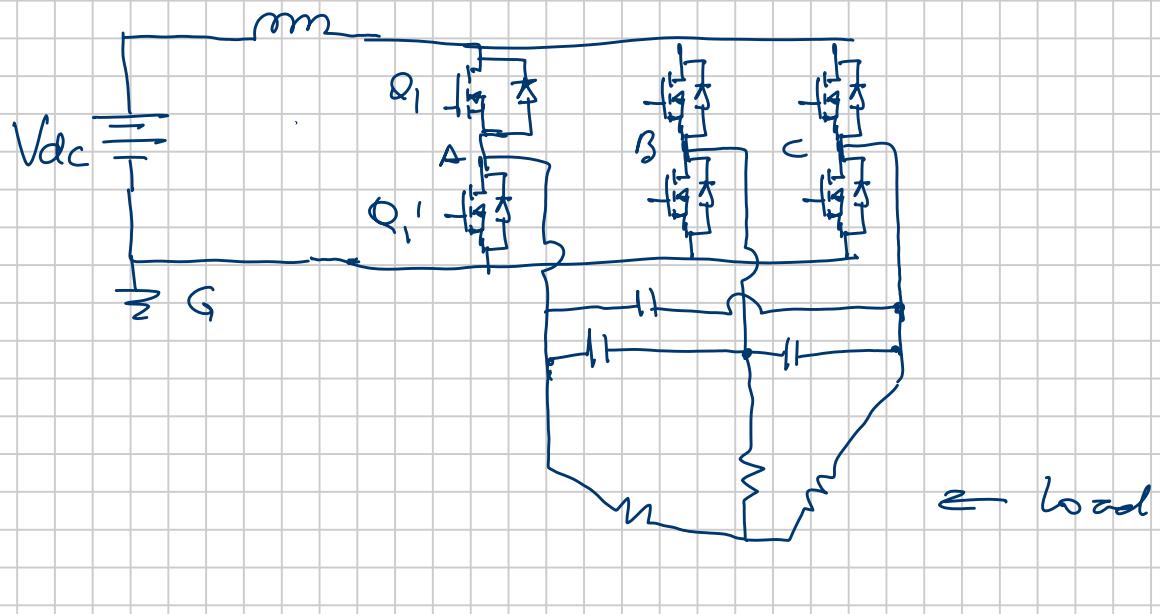

504

IEEE TRANSACTIONS ON INDUSTRY APPLICATIONS, VOL. 39, NO. 2, MARCH/APRIL 2003

Z-Source Inverter

Fang Zheng Peng, Senior Member, IEEE

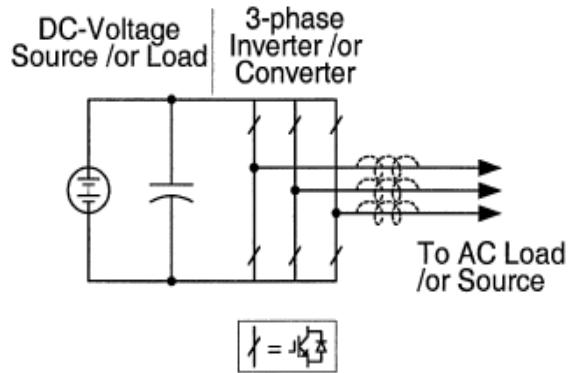


Fig. 1. Traditional V-source converter.

→ only reduces the input voltage

→ inconvenient output filter

→ only boost input voltage

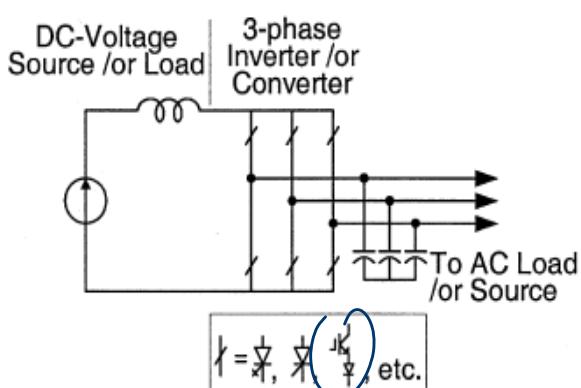


Fig. 2. Traditional I-source converter.

→ Requires additional diode to block

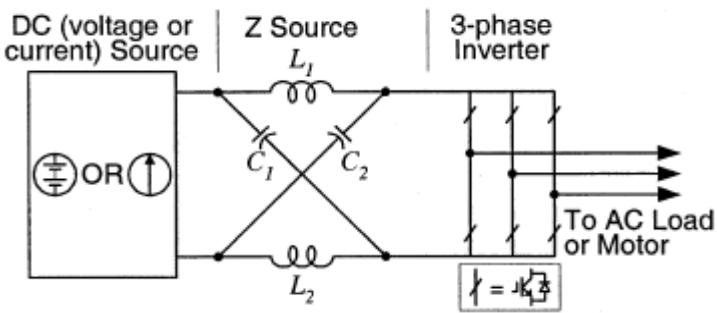


Fig. 4. Z-source converter structure using the antiparallel combination of switching device and diode.

Impedance source converter
→ ZSI

Can both buck and boost voltage

Boost factor → depends on the ratio between shoot-through and non-shoot-through states

$$V_{out \text{ fund freq ph}} = m_B \frac{V_{dc}}{2}$$

mod index

$$m_B = B_3$$

Buck-Boost factor

Can vary between 0.1

2:1 range

in fuel cells

typical dc link voltage

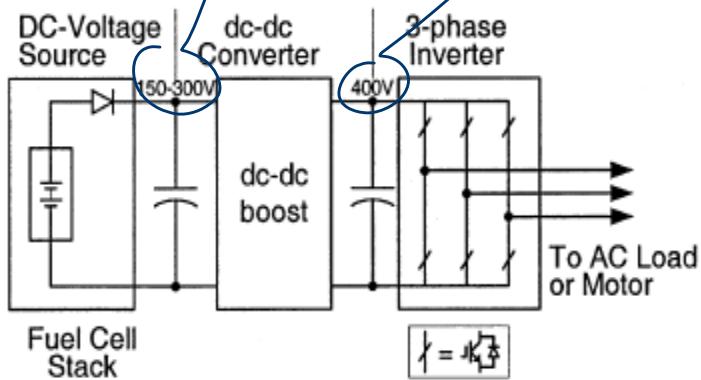


Fig. 6. Traditional two-stage power conversion for fuel-cell applications.

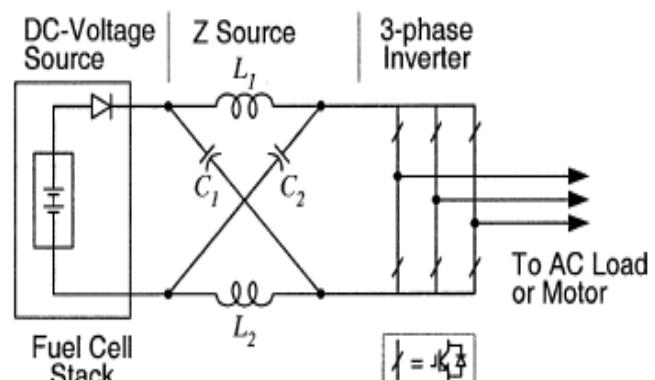


Fig. 7. Z-source inverter for fuel-cell applications.

