

Lecture 4 Arithmetic-Logic Unit

Arithmetic - Logic Unit ALU

- ❑ Handles integers
- ❑ Does the calculations

Arithmetic-Logic Unit ALU

- ❑ **Performs arithmetic**
add, subtract
- ❑ **Performs logic**
and, or, invert, complement
- ❑ **Shifts**
right, left, arithmetic, logical
- ❑ **Provides result and status**

Review Binary Addition

	Binary					Decimal		
Carry	1	1	1	1	0	0	0	
		1	1	0	1	1	2	7
		1	0	1	1	0	2	2
	1	1	0	0	0	1	0	4
							9	

Example Numbers

□ 8 bit 2's complement

$$+127 = 01111111 = 2^7 - 1$$

$$-128 = 10000000 = -2^7$$

□ 16 bit 2's complement

$$+32767 = 01111111 11111111 = 2^{15} - 1$$

$$-32768 = 10000000 00000000 = -2^{15}$$

Sign Extension

- ❑ Positive number pack with leading zeros

+18 = 00010010

+18 = 00000000 00010010

- ❑ Negative number pack with leading ones

-18 = 11101110

-18 = 11111111 11101110

- ❑ i.e. pack with **MSB** (sign bit)


Addition and Subtraction

- ❑ Normal binary addition circuitry
- ❑ Take two's complement of subtrahend and add to minuend
i.e. $a - b = a + (-b)$
- ❑ Need only addition and complement circuits

Consider Binary Addition

Assume 5 bits **2's complement arithmetic**

$$12 - 7 = 12 + (-7) = 5$$

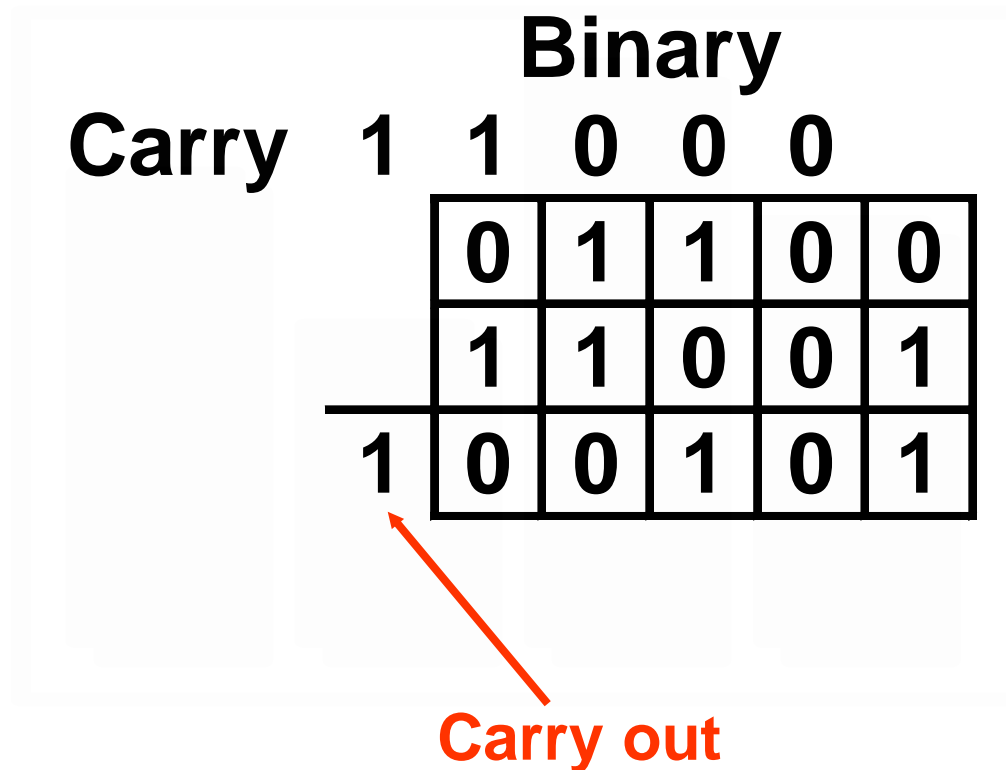

Consider Binary Addition

Assume 5 bits **2's complement arithmetic**


$$12 - 13 = 12 + (-13) = -1$$

Binary

Carry	0	0	0	0	0
	0	1	1	0	0
	1	0	0	1	1
	0	1	1	1	1


Carry out

ALU Inputs and Outputs

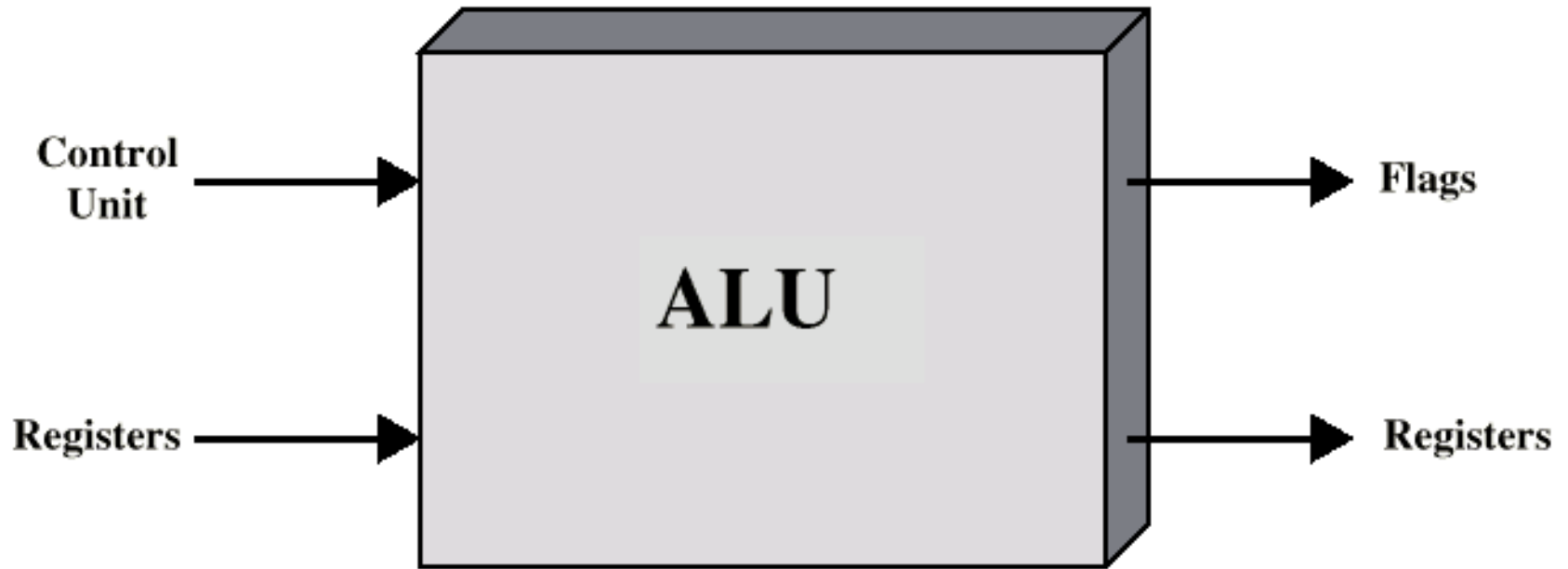


ALU - Addition

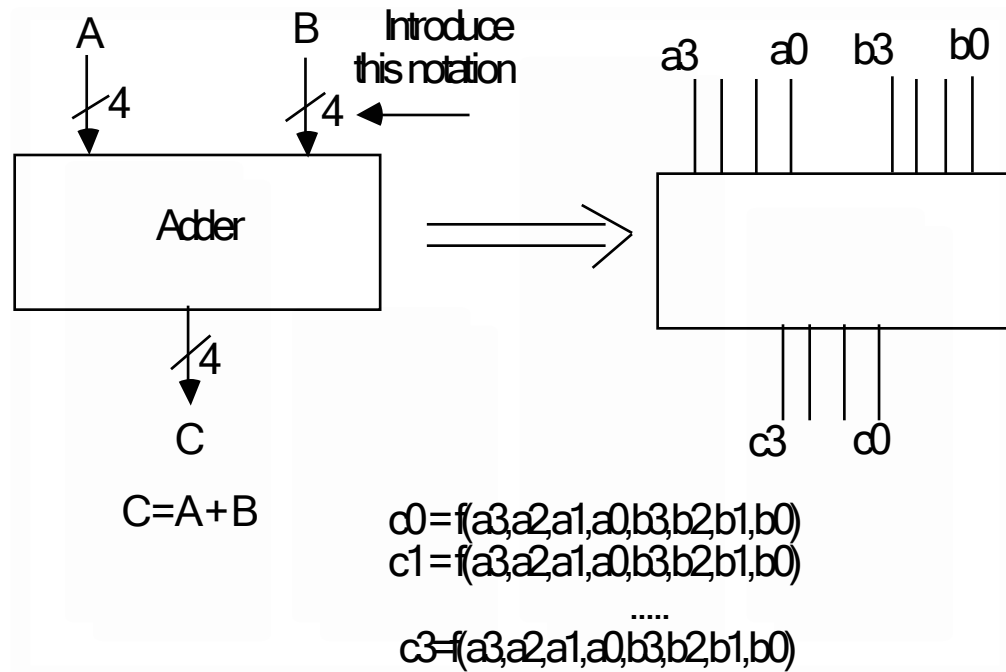Could try this as an 8 input, 4 output combinational logic problem



Instead - Consider Stages

FA - Full Adder

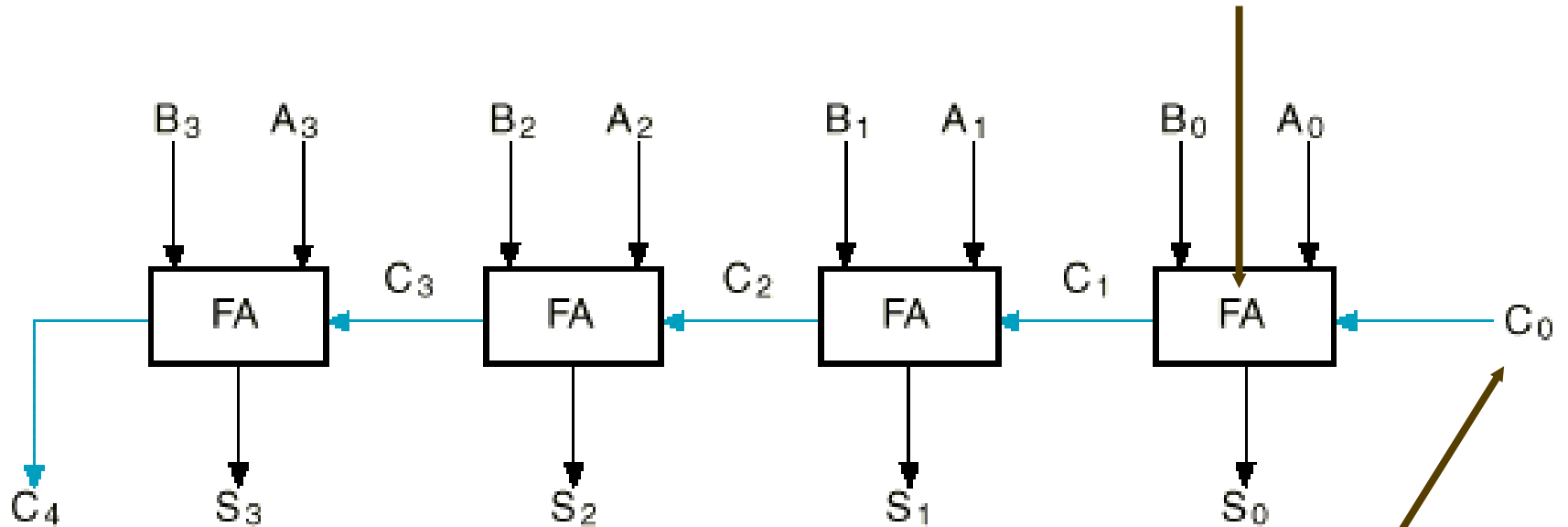

Depends on 1's or 2's comp arithmetic

Full Adder


Truth Table

A	B	C _{in}	S	C
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1


$$\begin{aligned} S &= A'B'C_{in} + A'BC_{in}' + \\ &\quad AB'C_{in}' + ABC_{in} \\ &= A \oplus B \oplus C_{in} \end{aligned}$$

$$\begin{aligned} C &= A'BC_{in} + AB'C_{in} + \\ &\quad ABC_{in}' + ABC_{in} \\ &= (A \oplus B)C_{in} + AB \end{aligned}$$

Full Adder

 

4 Bit Ripple Carry 2's Complement Adder

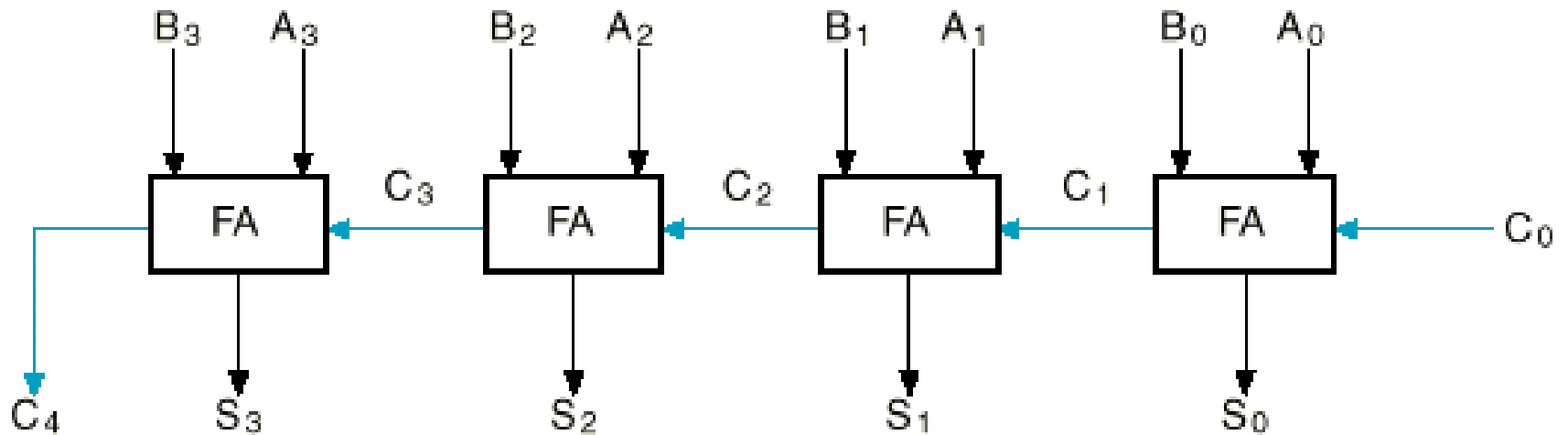


Constructing an Arithmetic Logic Unit

Start with a 1-Bit ALU


Simple Logical Operations

1. AND gate ($c = a \cdot b$)

 


a	b	$c = a \cdot b$
0	0	0
0	1	0
1	0	0
1	1	1

2. OR gate ($c = a + b$)

 


a	b	$c = a + b$
0	0	0
0	1	1
1	0	1
1	1	1

3. Inverter ($c = \bar{a}$)

 


a	$c = \bar{a}$
0	1
1	0

 4. Multiplexor \square
 (if $d = 0$, $c = a$; \square
 else $c = b$)




d	c
0	a
1	b

Starting from “AND” and “OR”

 


If Operation is 0, then Result = a AND b
If Operation is 1, then Result = a OR b

Consider a 1 bit Full Adder

 

With “add”

 If Op is 0, then Result = a AND b
If Op is 1, then Result = a OR b
If Op is 2, then Result = sum of (a + b)




If we repeat the 1-Bit ALU 32 times

If Op is 0, then $Res_i = a_i \text{ AND } b_i$

If Op is 1, then $Res_i = a_i \text{ OR } b_i$

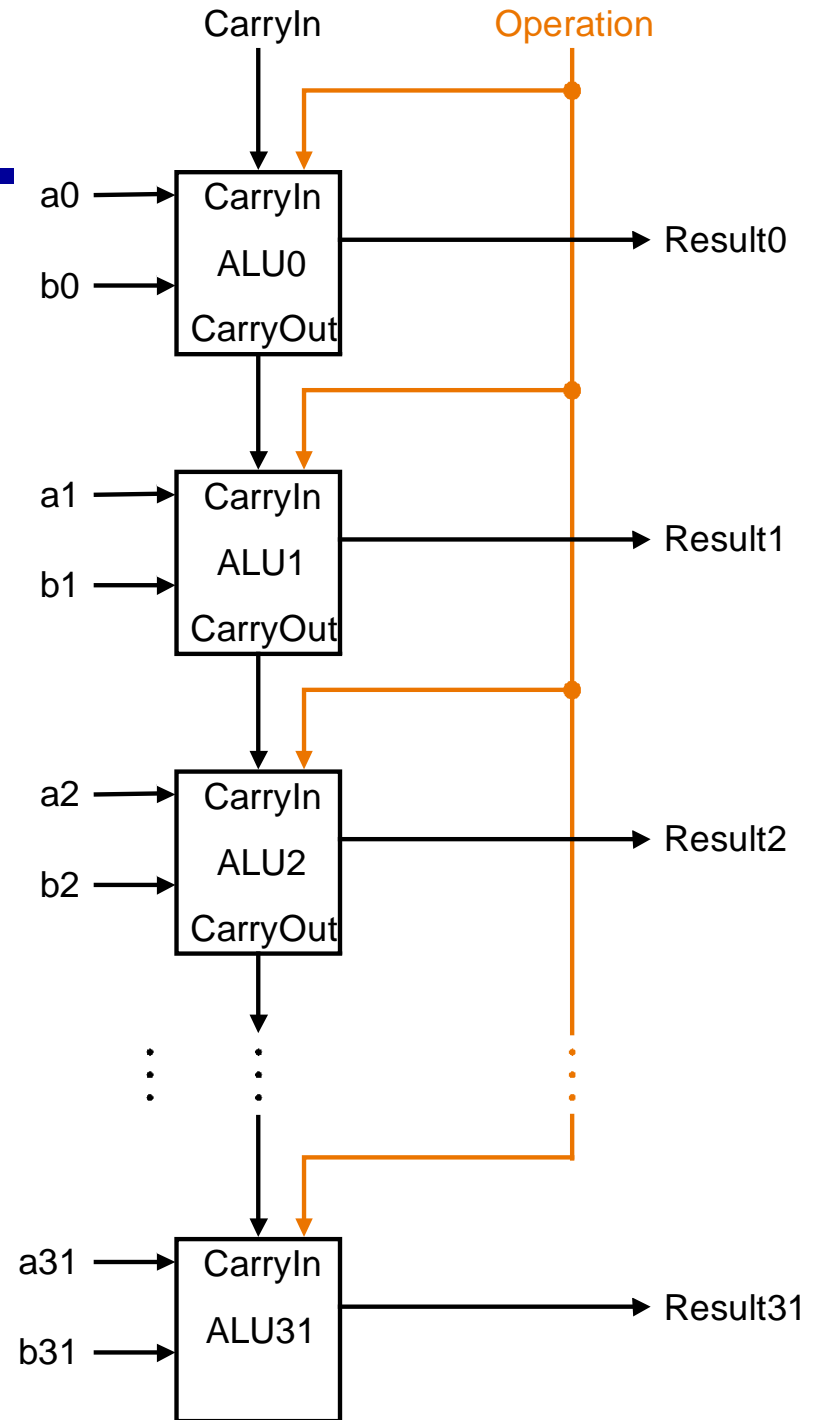If Op is 2, then $Res_i = \text{sum of } (a_i + b_i)$



With Subtraction

If Op is 0, then Res = a AND b

If Op is 1, then Res = a OR b

If Op is 2,

and if Binvert is 0,


then Res = sum (a + b)

if Binvert is 1,

then Res = sum (a + (-b))


Note that (- b) is 1's comp

Add a 1 into CarryIn₀ to get 2's comp

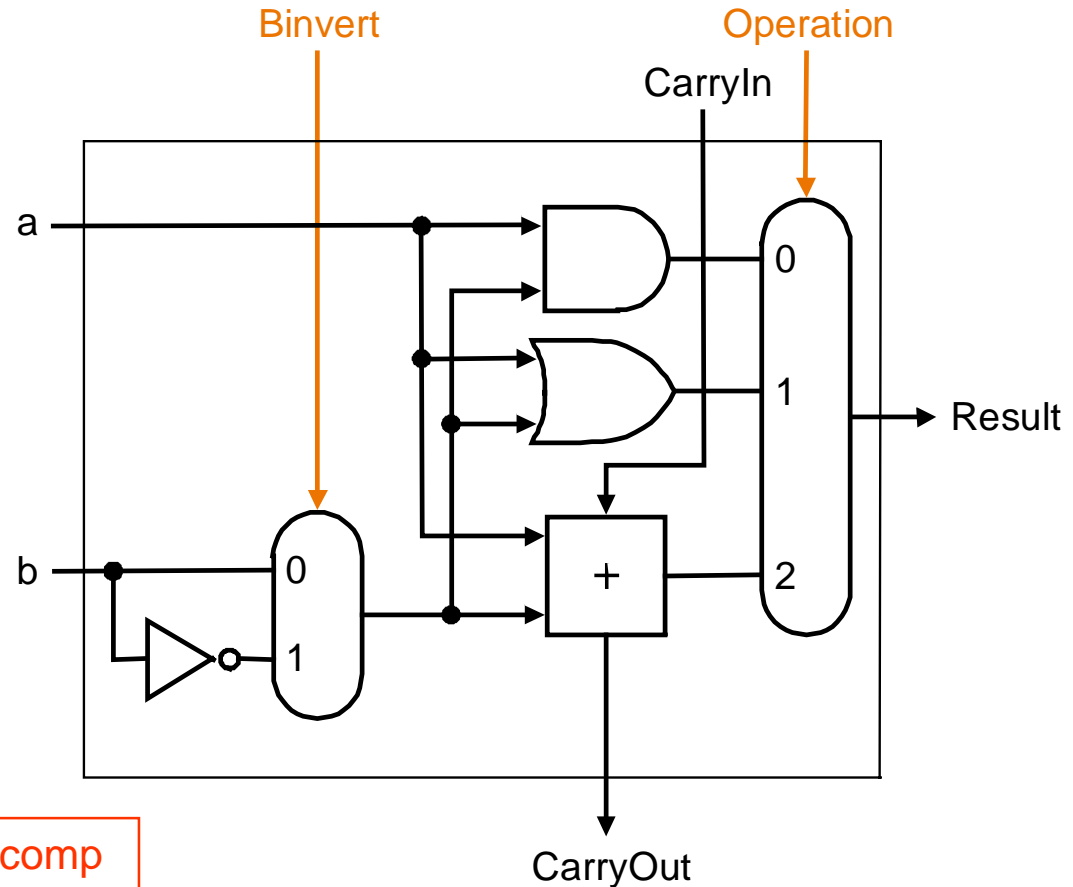

ALU with Zero Detection — for comparing a and b

Control Lines	Function
000	and
001	or
010	add
110	sub

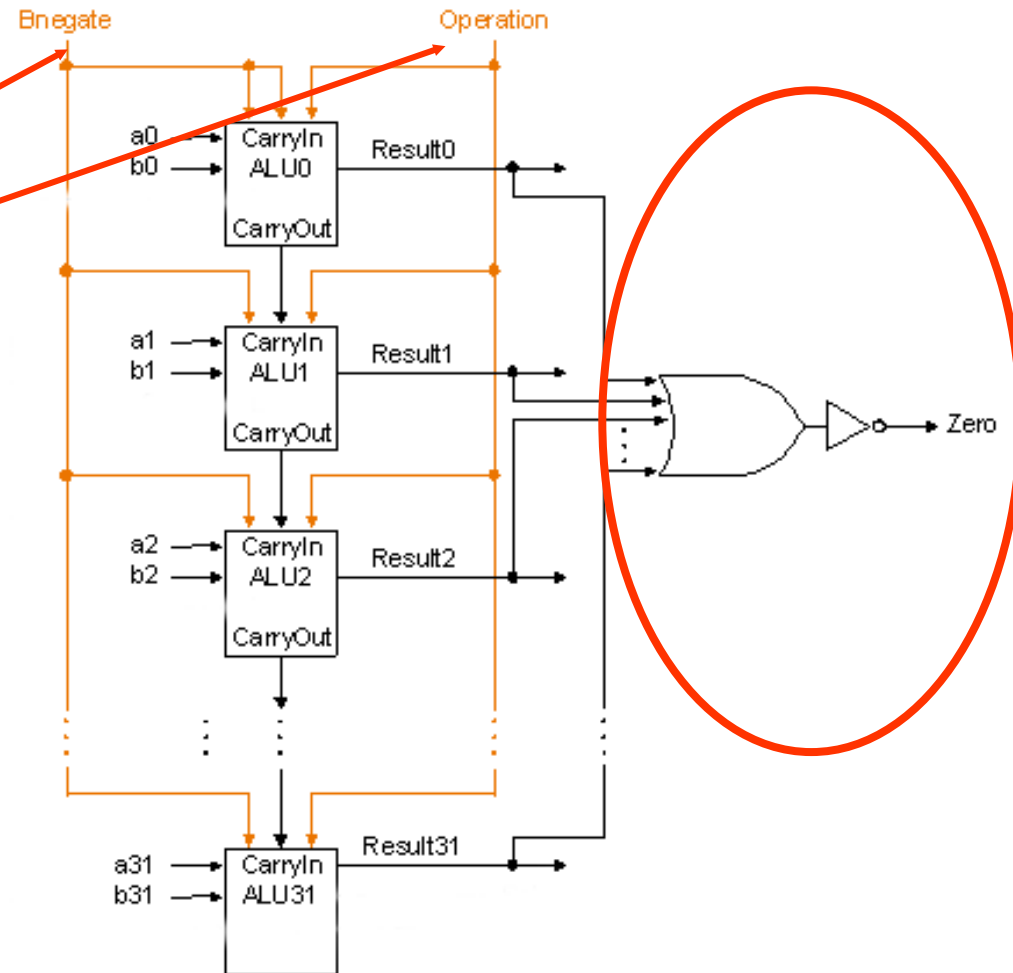

Overflow

□ Result too large for finite computer word:


- e.g., adding two n-bit numbers does not yield an n-bit number

$$\begin{array}{r} 0111 \\ + 0001 \\ \hline 1000 \end{array} \quad \begin{array}{l} \textit{note that overflow term is somewhat misleading,} \\ \textit{it does not mean a carry "overflowed"} \end{array}$$

Detecting Overflow

- ❑ No overflow when adding a positive and a negative number
- ❑ No overflow when signs are the same for subtraction
- ❑ Overflow occurs when the value affects the sign:
 - overflow when adding two positives yields a negative
 - or, adding two negatives gives a positive
 - or, subtract a negative from a positive and get a negative
 - or, subtract a positive from a negative and get a positive
- ❑ Consider the operations $A + B$, and $A - B$
 - Can overflow occur if B is 0 ?
 - Can overflow occur if A is 0 ? Yes

Example Overflow Logic

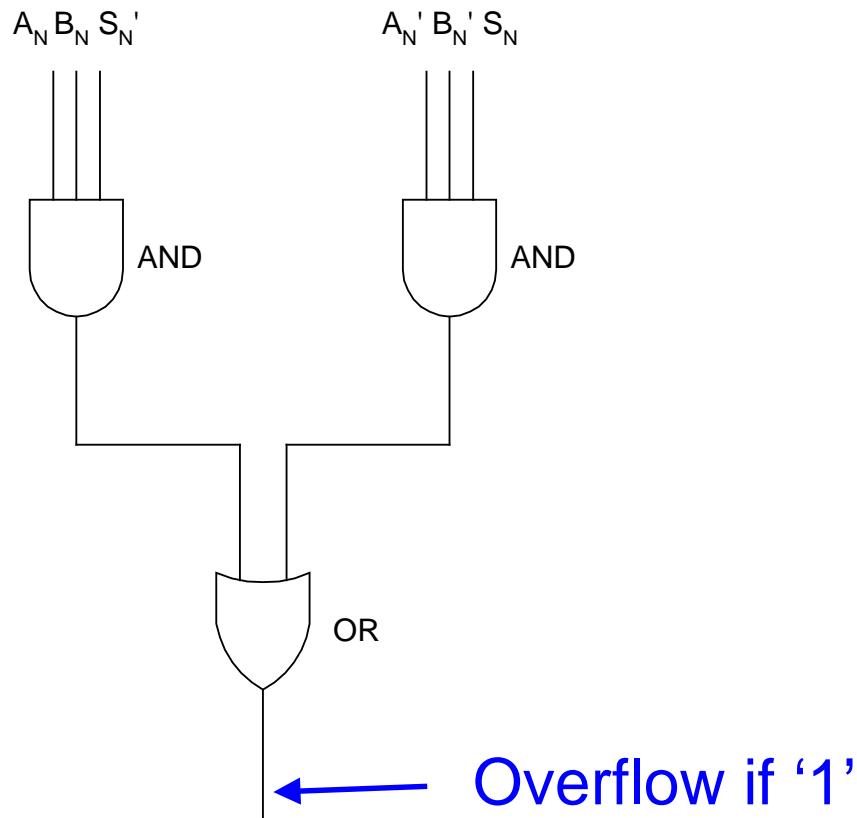


How is this derived? – Homework!


Effects of Overflow

- ❑ **An exception (interrupt) occurs**
 - Control jumps to predefined address for exception
 - Interrupted address is saved for possible resumption
- ❑ **Details based on software system / language**
 - example: flight control vs. homework assignment
- ❑ **Don't always want to detect overflow**
 - MIPS instructions: `addu`, `addiu`, `subu`
 - More later


Common Symbol for ALU

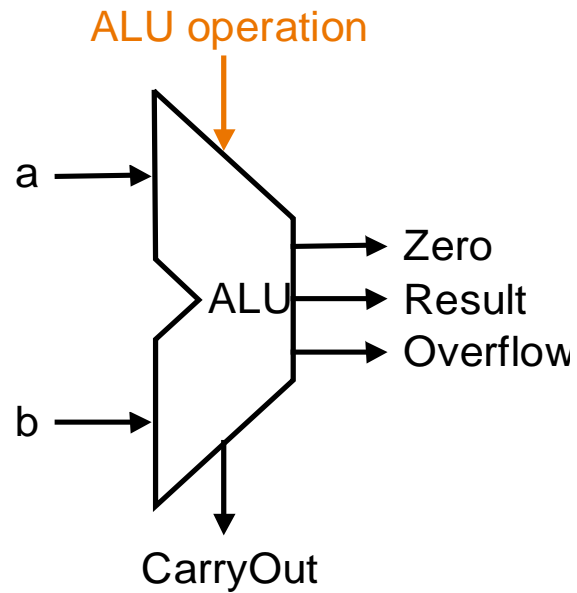

Recall Full Adder

 


Full Adder - Half Adders

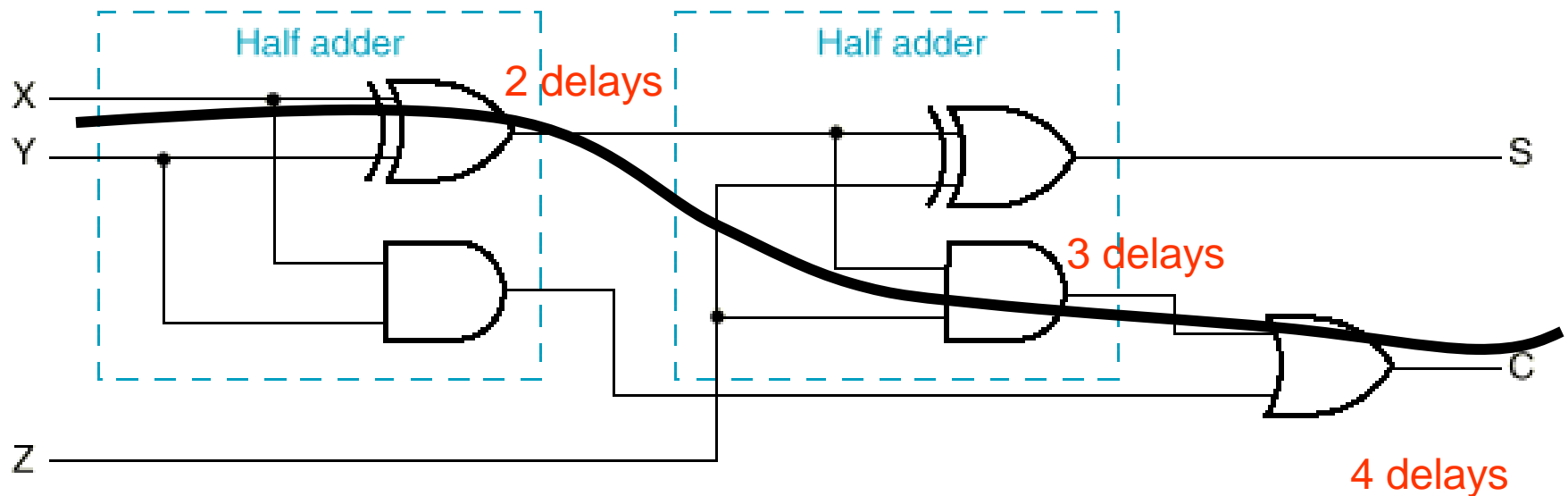

From Z to C is 2 delays for each subsequent stage or $2N + 2$

4 Bit Ripple Carry Adder

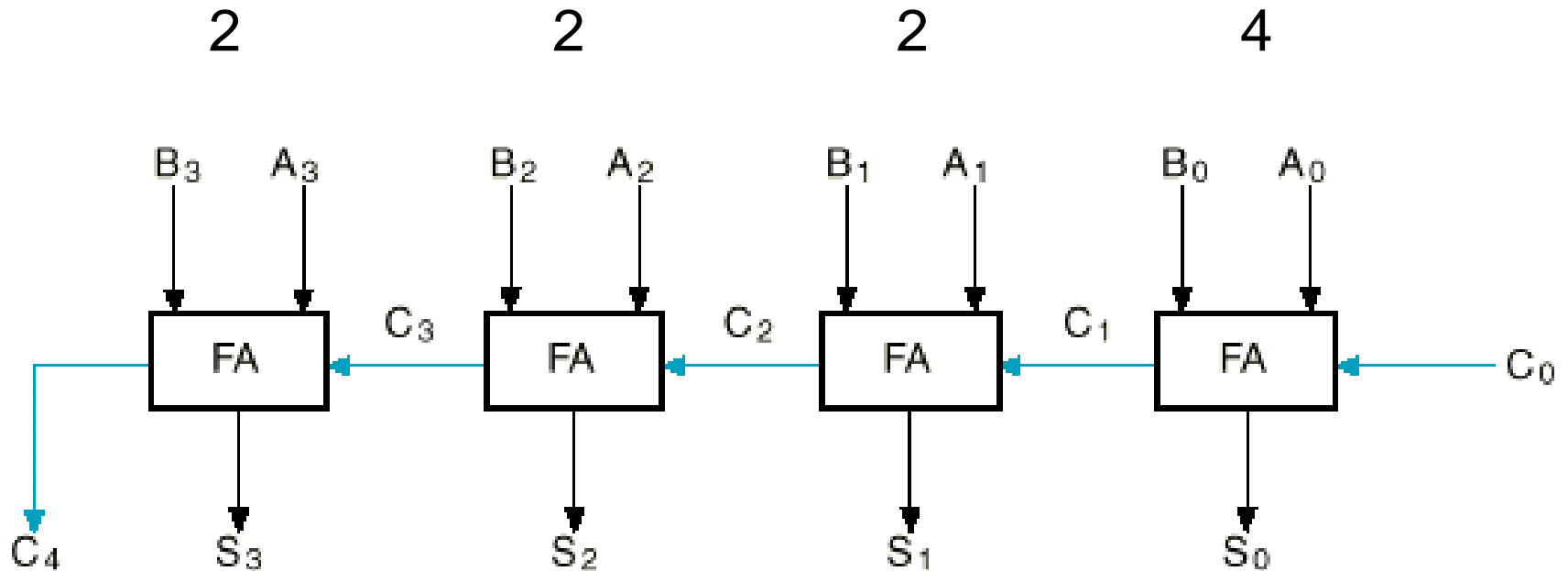

$2n+2$ gate delays (10) for 2's complement

Carry Lookahead Equations

Let $g_i = a_i b_i$
 $p_i = a_i + b_i$

generating carry
propagating carry

$$c_1 = b_0 c_0 + a_0 c_0 + a_0 b_0$$

$$c_1 = g_0 + p_0 c_0$$

$$c_2 = b_1 c_1 + a_1 c_1 + a_1 b_1$$


$$c_2 = g_1 + (p_1 g_0) + (p_1 p_0 c_0)$$

$$c_3 = b_2 c_2 + a_2 c_2 + a_2 b_2$$

$$c_3 = g_2 + p_2 g_1 + (p_2 p_1 g_0) + (p_2 p_1 p_0 c_0)$$

$$c_4 = b_3 c_3 + a_3 c_3 + a_3 b_3$$
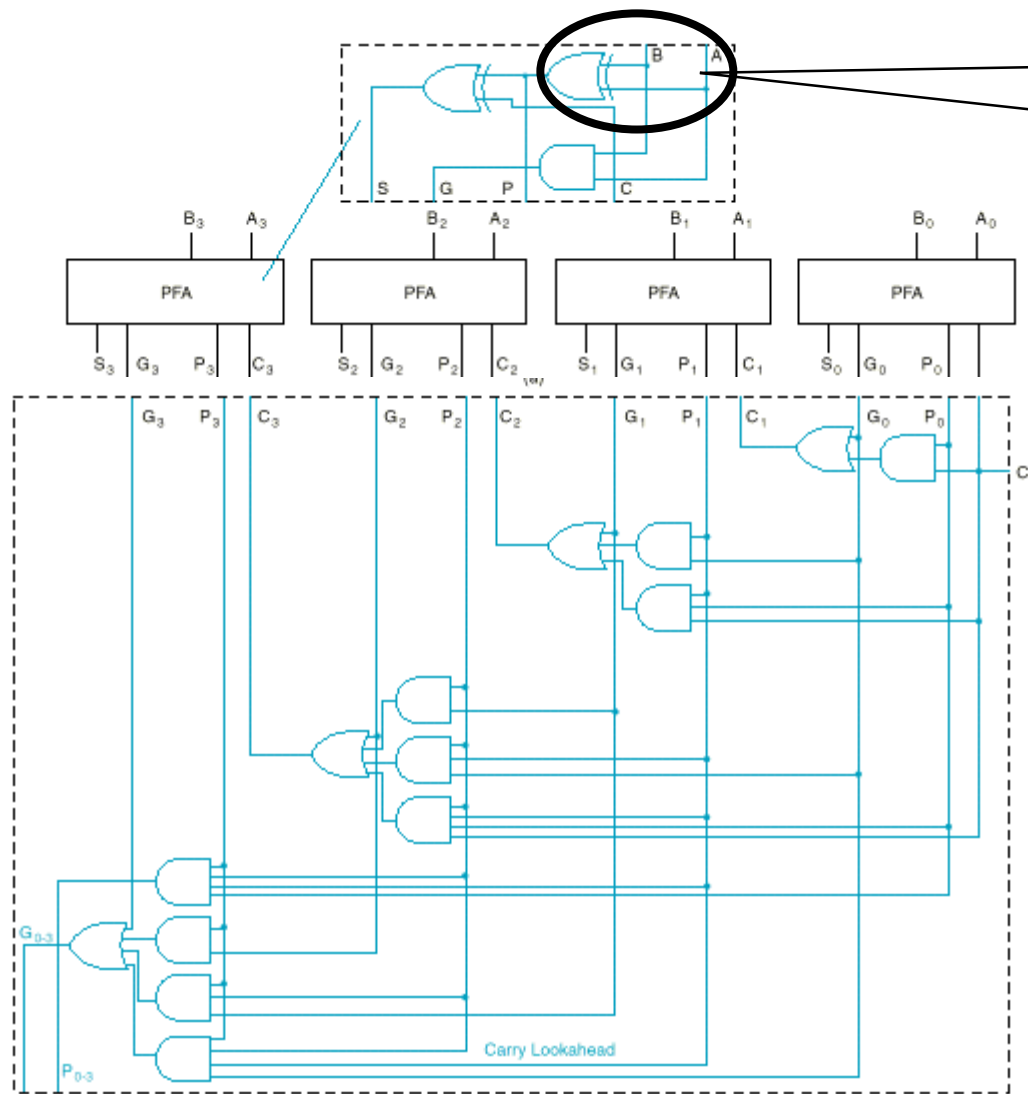
$$c_4 = \underbrace{g_3 + p_3 g_2 + p_3 p_2 g_1 + (p_3 p_2 p_1 g_0)}_{G_{0-3}} + \underbrace{(p_3 p_2 p_1 p_0 c_0)}_{P_{0-3}}$$




Should be an OR gate.. What happened?

Reduces delay to 6 gate delays (from input to S)

4 gate delays from input to C

Carry Lookahead Adder

Carry Lookahead – Second Level

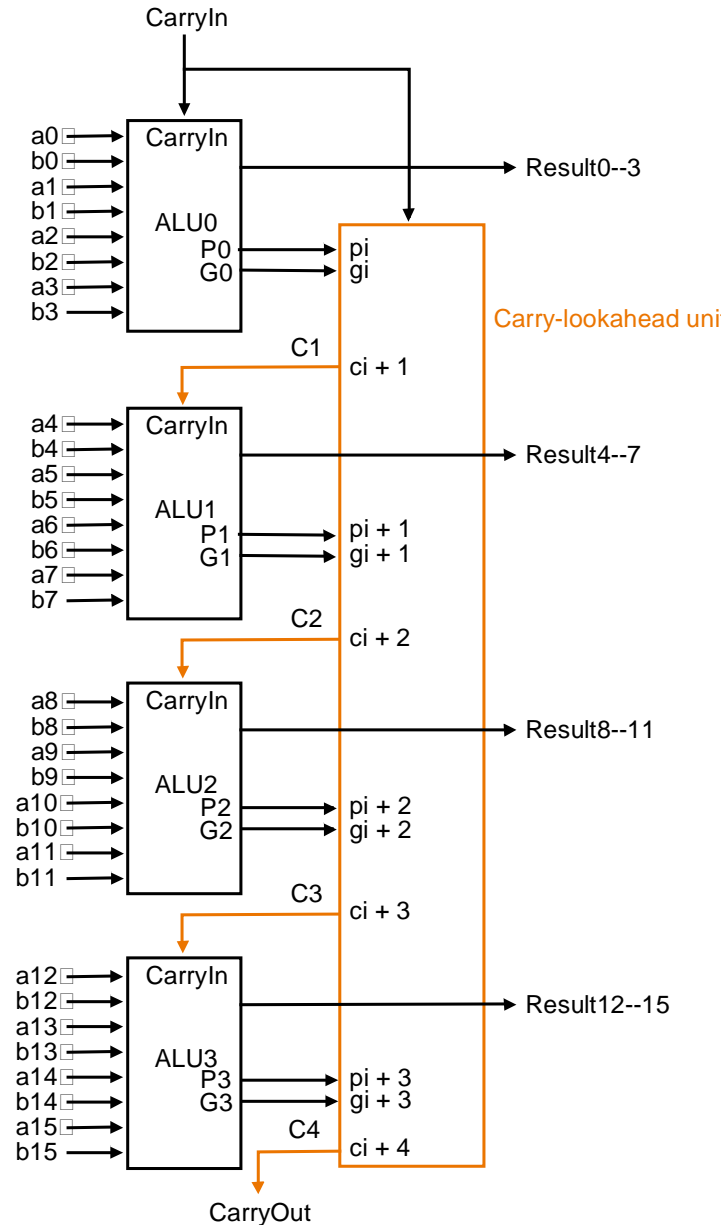

Carry Propagation

- ❑ 2's complement best
- ❑ 1's complement twice as long
- ❑ Significant delay reduction using Carry Look Ahead concept