

Transferring Data Among Registers


- **Point-to-Point Transfer**
 - **Serial Transfer: Shift Registers**
 - **Parallel Transfer**
 - **Control (Strobing Signal)**
 - **Clocking**
 - **Multiplexing**
- **Bus Transfer**
 - **Avoids Using Multiplexers**
 - **Destination Device is Selected**
 - **Registers are Interconnected With a Common Bus**

Martin B.H. Weiss

Register Transfer - 1

University of Pittsburgh

Serial Data Register Transfer

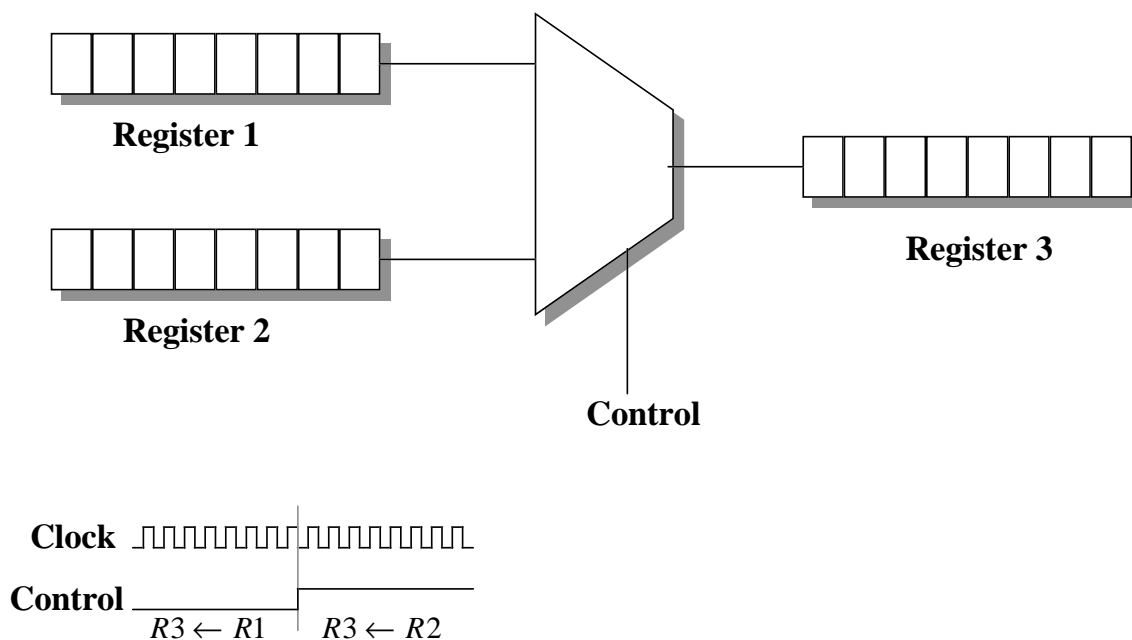


Martin B.H. Weiss

Register Transfer - 2

University of Pittsburgh


Parallel Data Transfer

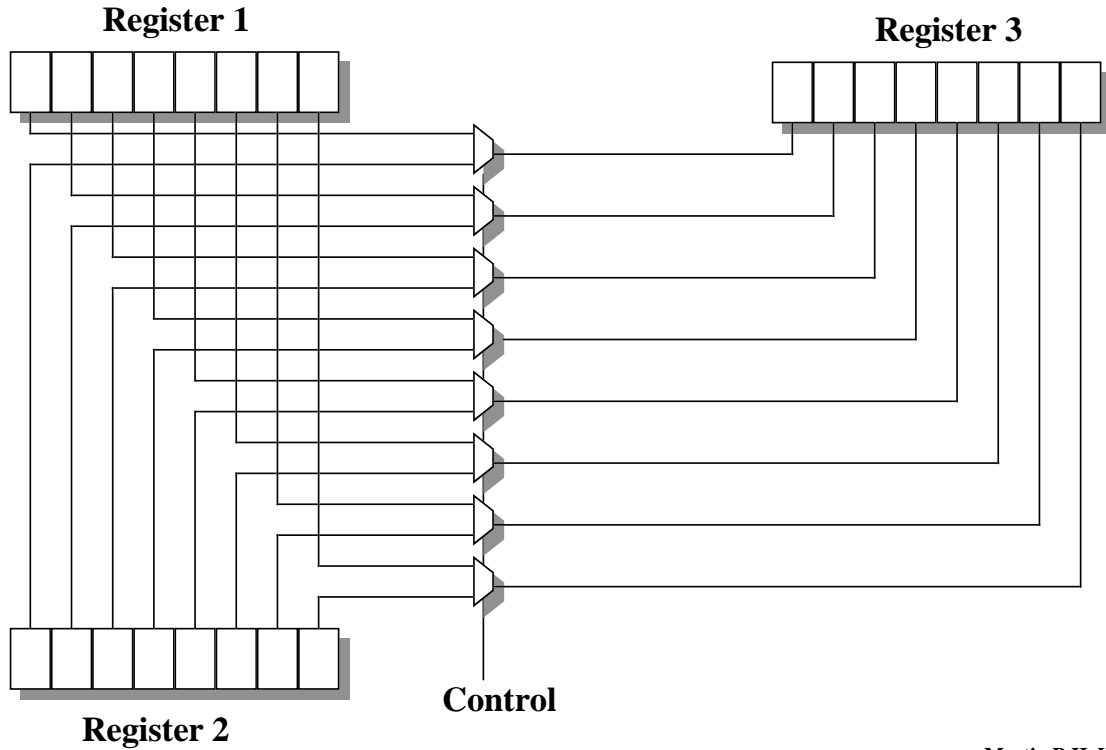

Register Transfer - 3

Martin B.H. Weiss
University of Pittsburgh

Parallel Data Transfer

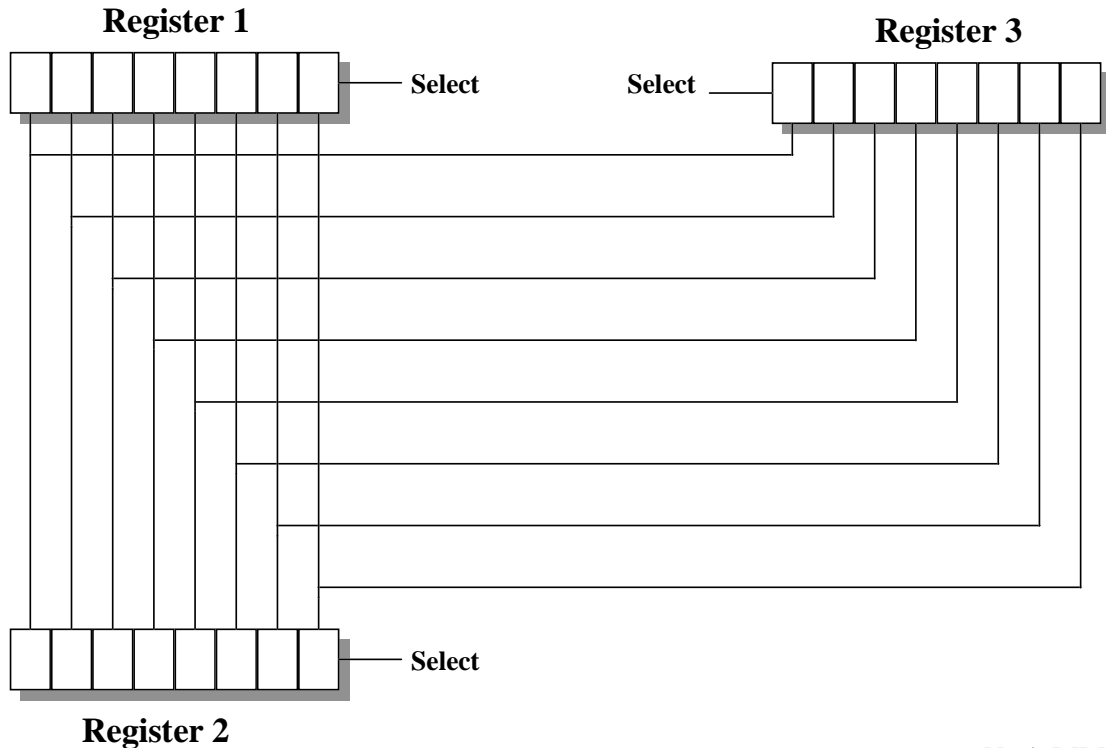

Register Transfer - 4

Martin B.H. Weiss
University of Pittsburgh

Register Transfer Definitions

- **A Register Is A Group of Flip-Flops Capable of Storing Information and Performing Simple Operations**
- **Micro-operation**
 - **Elementary Operation**
 - **Performed in Parallel on Data Stored in a Register**
 - **Performed in One Clock Period**
 - **Examples**
 - **Load**
 - **Shift Right**
 - **Shift Left**

Martin B.H. Weiss

Register Transfer - 5

University of Pittsburgh

Register Transfer Notation


- **Symbolic Method for Representing Information Flow Among Registers**
- **Examples**
 - **Register 2 Gets the Contents of Register 1: $R2 \leftarrow R1$**
 - **Register 2 Gets Part of Register 1: $R2(0-7) \leftarrow R1(8-15)$**
 - **Register 1 Gets Data at Memory Location AR: $R2 \leftarrow M[AR]$**

Martin B.H. Weiss

Register Transfer - 6

University of Pittsburgh

Hardware Structure

 

Transfer Notation

- **Need Multiplexer Control Leads**
- **Condition Register Transfer by State of the Control Leads**
- **Notation Examples**
 - $T_1 T_2: R0 \leftarrow R1$
 - $T_1' T_2: R0 \leftarrow R1$
- **External Control Logic Determines the Values of the Leads**
- **Need $\log_2 N$ Control Leads for N Multiplexers**

Application of Register Transfer

- **Formalization of Logic**
- **Translation of Hardware Design into Useful Operational Structures**
- **Stages of Representation**
 - **Hardware Schematic**
 - Can Produce Optimal Design
 - Difficult to Comprehend Operational Aspects
 - **Register Transfer Notation**
 - Simple Operational Formalization of Hardware Functionality
 - Needs Extension to be Useful
 - **Microoperations**
 - Extension of RTN
 - Building Blocks for ALU and CPU Functionality

Martin B.H. Weiss

Microoperations


- **Definition: Elementary Operation Performed on Registers in a Single Clock Cycle**
- **Classes**
 - **Register Transfer**
 - **Arithmetic**
 - **Logic**
 - **Register Shift**

Martin B.H. Weiss

Arithmetic Operations

- $R0 \leftarrow R1 + R2$ (Addition)
- $R0 \leftarrow R1 - R2$ (Subtraction)
- $R2 \leftarrow R2'$ (One's Complement)
- $R2 \leftarrow R2' + 1$ (Two's Complement)
- $R1 \leftarrow R1 + 1$ (Increment)
- $R1 \leftarrow R1 - 1$ (Decrement)

Arithmetic Hardware Structure

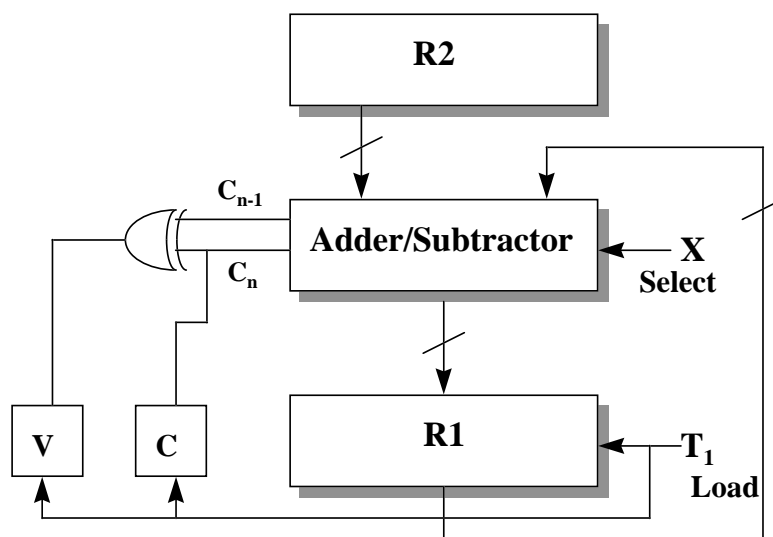

Logic Operations

- $R0 \leftarrow R0'$ (Complementation)
- $R0 \leftarrow R1 \wedge R2$ (AND)
- $R0 \leftarrow R1 \vee R2$ (OR)
- $R0 \leftarrow R1 \oplus R2$ (XOR)

Martin B.H. Weiss

Shift Operations

- $R \leftarrow \text{shl } R$
- $R \leftarrow \text{shr } R$
- $R \leftarrow \text{rol } R$
- $R \leftarrow \text{ror } R$
- $R \leftarrow \text{asl } R$
- $R \leftarrow \text{asr } R$
- Discussion
 - Shift: End Receives the Input From the Serial Input
 - Rotate: End Receives Shifted-Out Information (No Loss of Bits)

Martin B.H. Weiss

Arithmetic Shift

- **Left - Multiply a Signed Binary Number by 2**
- **Right - Divide a Signed Binary Number by 2**
- **Leave the Sign Bit Unchanged (R_{n-1})**
- **Negative Numbers**
 - **In Two's Complement Form**
 - **Sign Bit = 1**
 - **Insert a 0 Into the Vacated Bit**

Bus Transfer

- **Bus**
 - **Common Set of Parallel Wires (One for Each Bit) For All System Components**
 - **Also Contains Control Wires**
- **Operation**
 - **Device Outputs on the Bus Can Have Three States (1,0, High Impedance)**
 - **If the Device is Selected, the Output Must Be a 1 or a 0**
 - **If Not, the Output is High Impedance**
 - **Selection Done Via a Decoder**

Memory Transfer

- **Transfer Data From a Memory Location to a Register**
- **Address**
 - **Address Bus**
 - **Address Register (AR)**
 - **Bus Buffer**
- **Memory**
- **Data**
 - **Data Bus**
 - **Bus Buffer**
 - **Registers**