

# **Analysis and Design of Finite State Machines**

# Finite State Machines

The general class of circuits in which the output depends on past behavior are called **sequential circuits**

In most cases, a **clock signal** is used to control the operation of a sequential circuit (***synchronous sequential circuit***).

Synchronous sequential circuits are realized using combinational logic and flip-flops.

Sequential circuits are also referred to as **Finite State Machines (FSM)**

# FSM Design Example

Design a 3-bit synchronous Gray Code up/down counter using D Flip-Flops and gates

## 1. Sequence

$Q_2$									
$Q_1$									
$Q_0$									
State									

## 2. Up/Down Control

## 3. Synchronous

# State Transition Diagrams

The **State** of the circuit is defined by the Q outputs of the flip-flops.

**State transition Diagrams** show states and possible from one state to another

# State Transition Table

**State Transition Tables** are truth tables that show for each combination of state and inputs, what the Next State will be.

<i>R</i>	<i>Present state</i>			<i>Next state</i>		
	<i>Q<sub>2</sub></i>	<i>Q<sub>1</sub></i>	<i>Q<sub>0</sub></i>	<i>Q<sub>2</sub></i>	<i>Q<sub>1</sub></i>	<i>Q<sub>0</sub></i>


*For a counter, the output is the same as the state*

*For D Flip Flops, Q at the next state is equal to the value of D. Therefore, the Next State Columns show what the D inputs should be in this case*


# Next State Feedback Logic

We need to determine logical expressions for each flip-flop in terms of external inputs and the present state


$D_2$

 


$D_1$

 

$D_0$

 

# FSM Logic Implementation

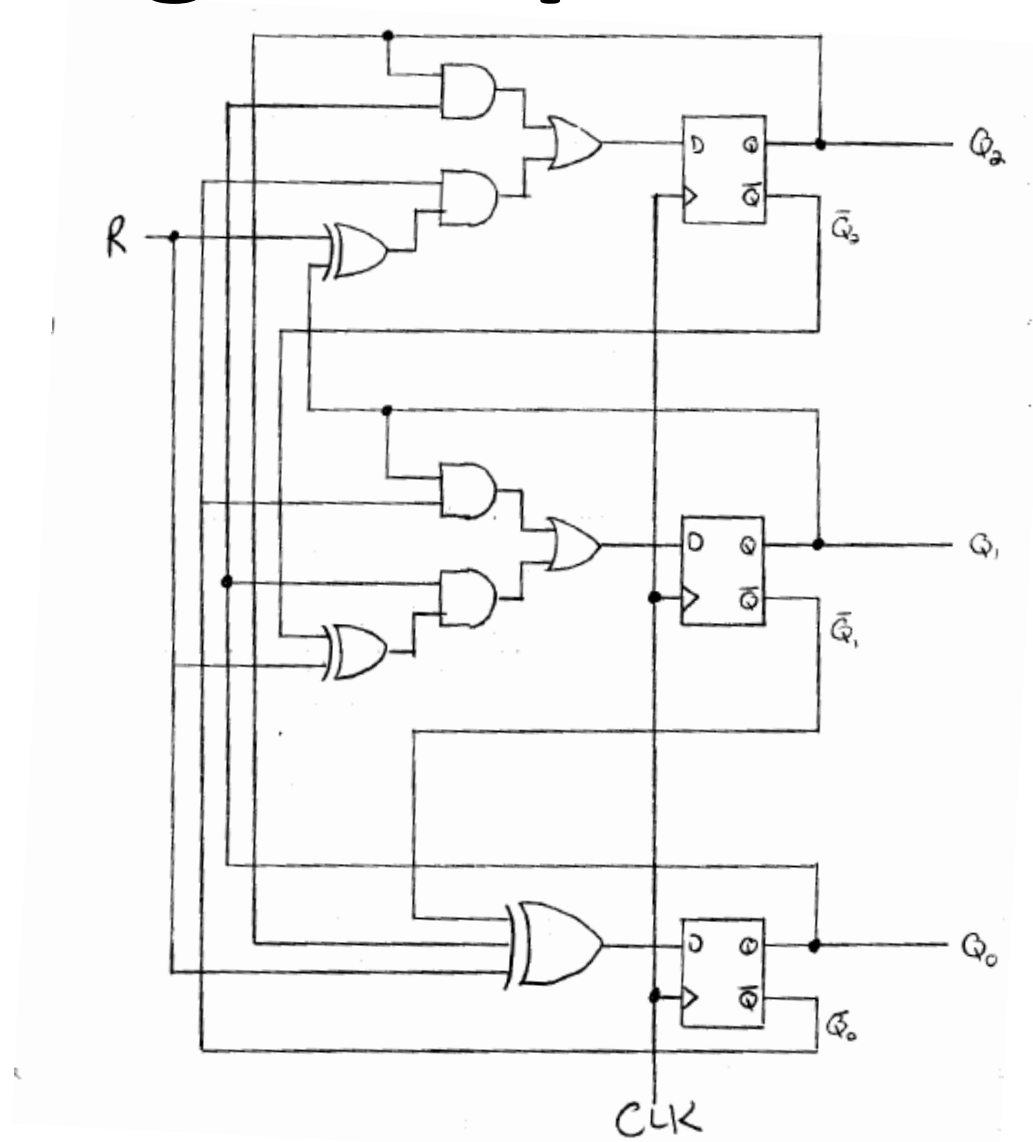

Schematic for 3 Bit Up/Down Gray Code Counter

# Finite State Machines

**Memory:** Flip-flops to store state values

**State Logic:** Logic network that takes the present state, inputs and produces signals that will drive the circuit to the next state

**Output Logic:** Produces Outputs Based on Present State (and possibly inputs)

***Moore Machine*** → Outputs depend only on **present state** (not inputs)

***Mealy Machine*** → Outputs depend on both the **present state AND inputs**



# FSM Design Example (II)

# 1. Specifications

## Design a circuit to meet the following specifications:

1. inputs  $w, \text{reset}, \text{clock}$ , one output  $z$
2. All changes in the circuit occur on the positive edge of the clock signal
3. The output  $z$  is equal to 1 if during the immediately preceding two clock cycles the input  $w$  was equal to 1. Otherwise the value of  $z$  is equal to 0
4.  $\text{resetn} = 0$  puts the circuit into its default state where  $z = 0$  (Active Low Asynchronous Reset)

[illegible]


# FSM Design Example (II)

## 2. State Transition Diagram

# FSM Design Example (II)


## 3. Draw the State Table

Present state	Next state	Output $z$
A		
B		
C		

 

# FSM Design Example (II)

## 4. State Assignment

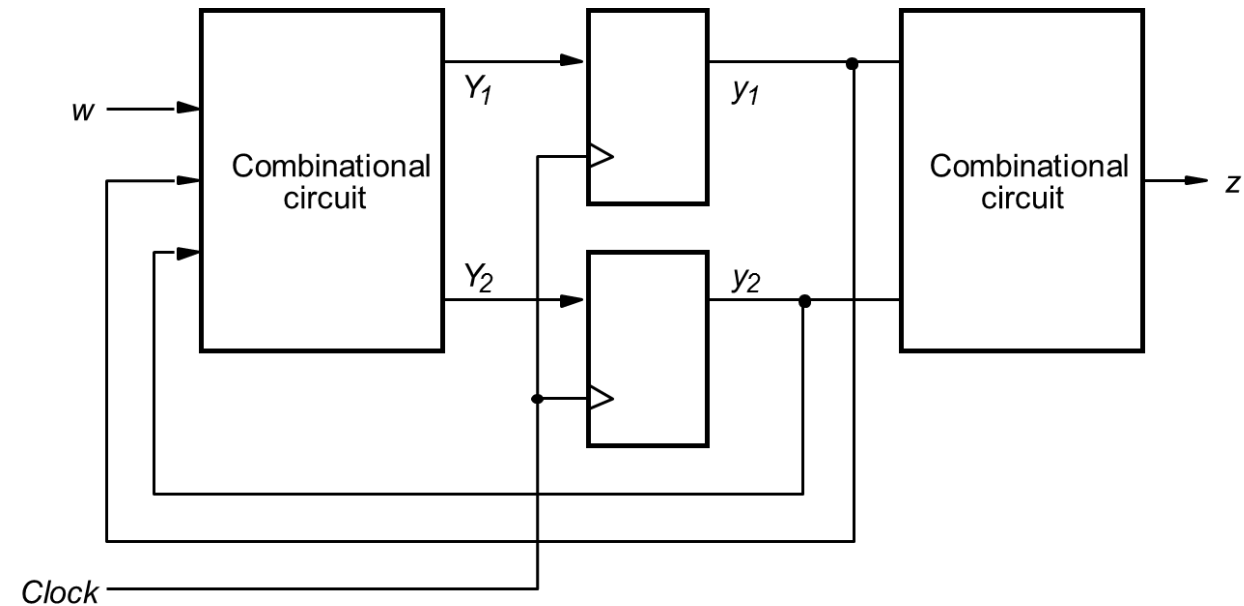

Present state $y_2 y_1$	Next state		Output $z$
	$w = 0$	$w = 1$	
	$Y_2 Y_1$	$Y_2 Y_1$	

# FSM Design Example (II)

## 5. Derive Next-State and Output Expressions

### Next State Expressions

		$Y_1$				
		$y_2 y_1$	00	01	11	10
$w$	0					
	1					


		$Y_2$			
		$y_2 y_1$	00	01	11
$w$	0				
	1				

### Output Expressions

		<b>Z</b>	
		$y_1$	
$y_2$	0		
	1		



# FSM Design Example (II)

6. Draw the schematic

 

# FSM Design Example (II)

## 6. Timing Diagram Verification

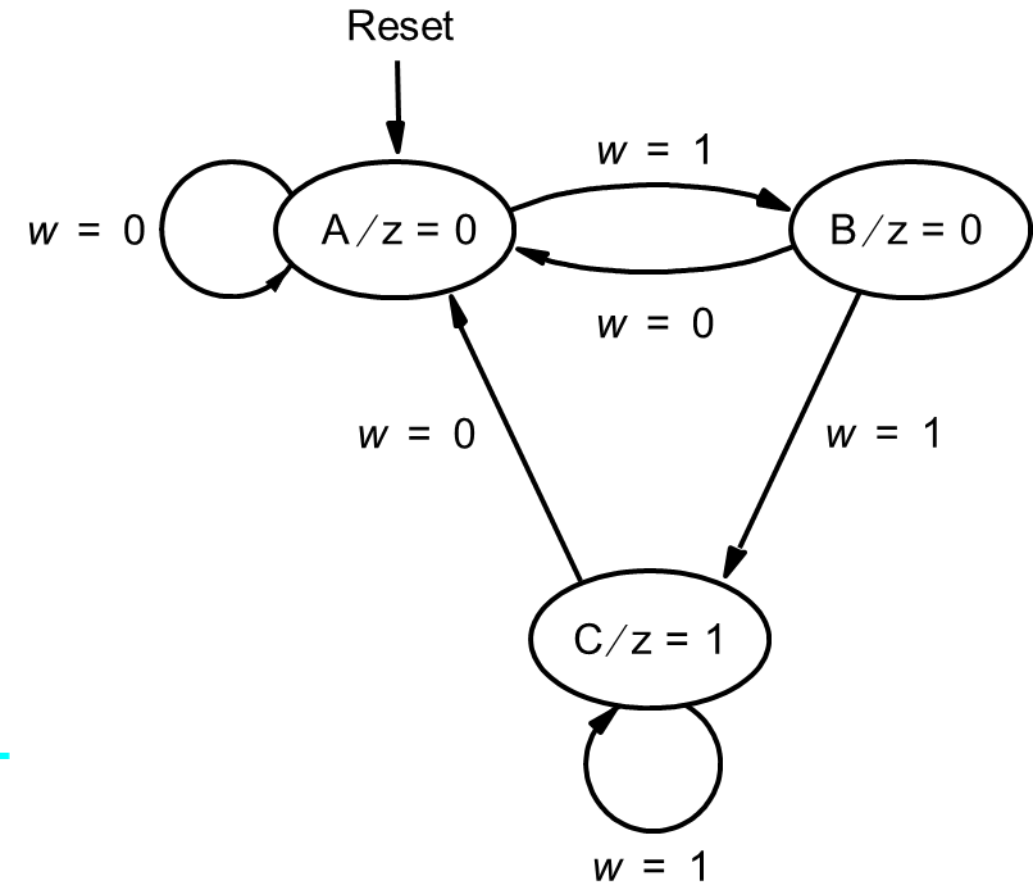 

# FSM Analysis Example: Determine how the sequential circuit below operates


## 1. FSM Type

## 2. State Logic

### 3. Output Logic

#### 4. State Transition Table

Include “Excitations”: Show flip-flop inputs produced by state logic, use them to determine Next State

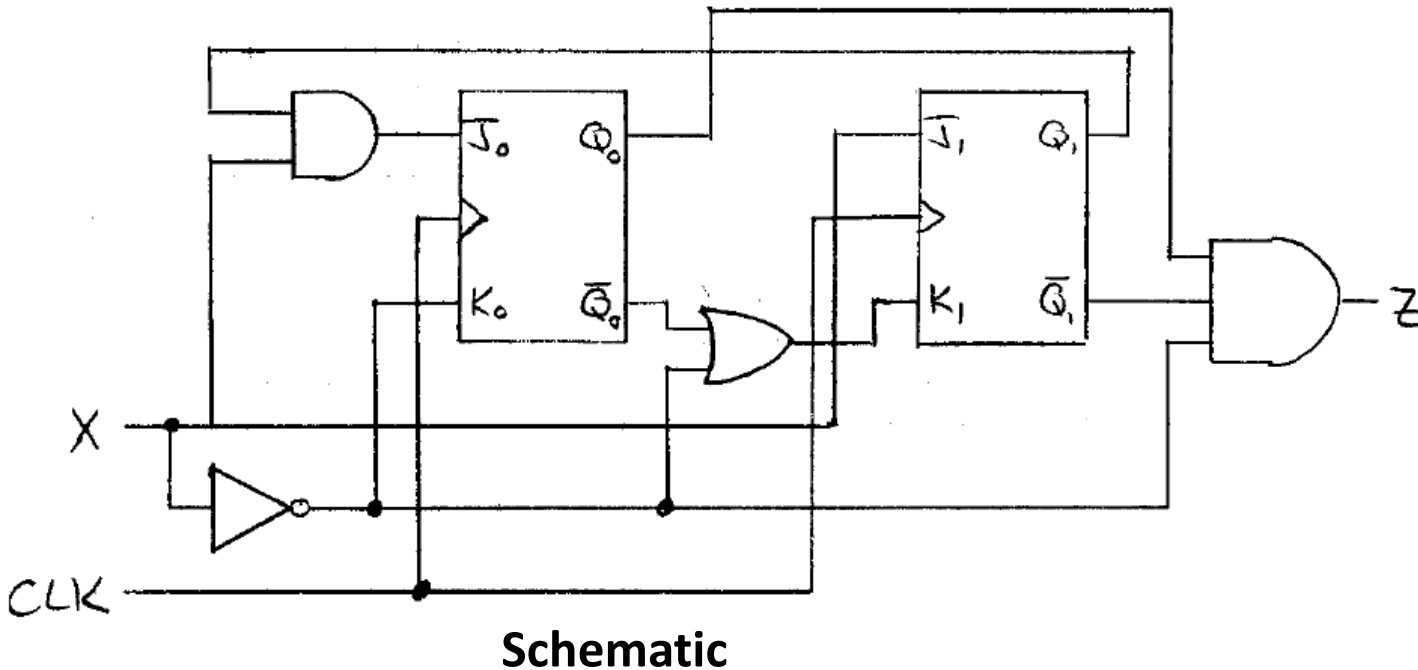[illegible]



# FSM Analysis Example

## 5. State Diagram

Mealy Notation → Input / Output on transitions

## 6. Behavioral Description

*From any State, go to State 0 if  $X = 0$*

*Can only reach State 2 from State 0 when  $X = 1$*

*Can only reach State 1 from State 2 when  $X = 1$*

*Reach State 3 from either State 1 or State 3 when  $X = 1$*

## 7. I/O Example

<b>X</b>	0	1	0	0	1	1	0	1	1	0	1	1	1	0	0	1	1	0	0	1
<b>Z</b>	0	0	0	0	0	0	1	0	0	1	0	0	0	0	0	0	0	1	0	0

*$Z = 1$  only when in State 1 and  $X = 0$*