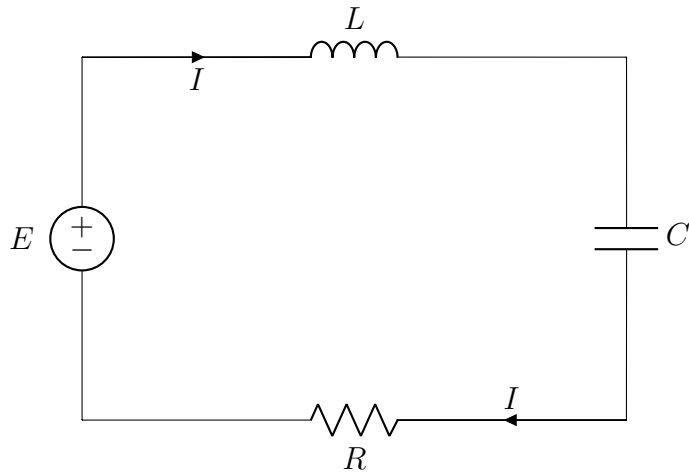


3.4 Electrical Circuits:



An RLC circuit.

E is the voltage source (voltage drop in V, volts)

R is the resistor (resistance in Ω , ohms)

C is the capacitor (capacitance in F, farads)

L is the inductor (inductance in H, henrys)

I is the current (in A, amperes)

Component laws:

1. Ohm's law: $E_R = RI$

2. Faraday's law: $E_L = L \frac{dI}{dt}$

3. Capacitance law: $E_C = \frac{Q}{C}$ Q is the charge on the capacitor (in C, coulombs)

4. Kirchhoff's voltage law: The sum of the voltage drops around any closed loop in a circuit must be zero.

5. Kirchhoff's current law: The sum of currents flowing into any junction is zero.

From the law 4 we get $E_L + E_C + E_R - E = 0$ or

$$L \frac{dI}{dt} + \frac{Q}{C} + RI = E \quad (1)$$

We use $I = \frac{dQ}{dt}$ and differentiate (1) to get

$$L \frac{d^2I}{dt^2} + \frac{1}{C} \frac{dQ}{dt} + R \frac{dI}{dt} = \frac{dE}{dt} \quad (2)$$

or

$$L \frac{d^2I}{dt^2} + R \frac{dI}{dt} + \frac{1}{C} I = \frac{dE}{dt} \quad (3)$$

If there is no capacitor then from (1) we obtain

$$L \frac{dI}{dt} + RI = E \quad (4)$$

If there is no inductor then $RI + \frac{Q}{C} = E$ or

$$R \frac{dQ}{dt} + \frac{Q}{C} = E \quad (5)$$

Example 1: $R = \frac{1}{2} \Omega$, $L = 1\text{H}$, $E = 1\text{V}$ and there is no capacitor. If $I(0) = 0$ then find I .

Solution: The formula (4) gives the IVP $\frac{dI}{dt} + \frac{1}{2}I = 1$, $I(0) = 0$.

It is a first order linear and separable equation. Its solution is $I(t) = 2(1 - e^{-t/2})$

Example 2: $R = 2 \Omega$, $C = \frac{1}{5} \text{F}$, $E = \cos t \text{V}$ and there is no inductor. Find I if $I(0) = 0$.

Solution: The formula (5) gives the IVP $2 \frac{dQ}{dt} + 5Q = \cos t$, $I(0) = 0$.

It is a first order linear equation. The integrating factor is $u(t) = e^{\int \frac{5}{2} dt} = e^{\frac{5}{2}t}$


Then $\left(e^{\frac{5}{2}t} Q\right)' = \frac{1}{2} e^{\frac{5}{2}t} \cos t \Rightarrow e^{\frac{5}{2}t} Q = \frac{1}{2} e^{\frac{5}{2}t} (2 \sin t + 5 \cos t) + C \Rightarrow$

$Q(t) = \sin t + \frac{5}{2} \cos t + C_1 e^{-\frac{5}{2}t} \Rightarrow I(t) = \frac{dQ}{dt} = \cos t - \frac{5}{2} \sin t + C e^{-\frac{5}{2}t}$

$I(0) = 1 + C = 0 \Rightarrow C = -1$

$I(t) = \cos t - \frac{5}{2} \sin t - e^{-\frac{5}{2}t}$

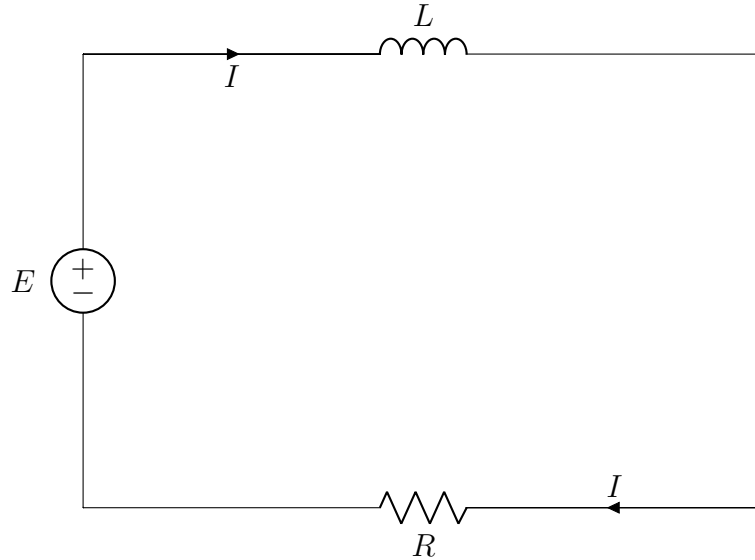- **Exercise #10, page 131.** An inductor ($1H$) and resistor (0.1Ω) are joined in series with an electromotive force (emf) $E = E(t)$ as in the Figure.



If there is no current in the circuit at time $t = 0$, find the ensuing current in the circuit at time t for the emf $E(t) = 4 \cos(3t) V$.

Solution: $L = 1H$ (Henry), $R = 0.1\Omega$,

$$E = E_R + E_L + \cancel{E_C} = RI + L \frac{dI}{dt} + \frac{1}{\cancel{C}} Q,$$

hence

$$4 \cos(3t) = 0.1I + 1 \frac{dI}{dt},$$

$$I' = -0.1I + 4 \cos(3t),$$

$$(Ie^{0.1t})' = 4 \cos(3t) \cdot e^{0.1t}, \quad Ie^{0.1t} = 4 \int \cos(3t) \cdot e^{0.1t} dt, \quad I(t) = 4e^{-0.1t} \int \cos(3t) \cdot e^{0.1t} dt. \quad (\cdot e^{0.1t})$$

Using integration by parts twice

$$I(t) = \frac{4}{901} (10 \cos(3t) + 300 \sin(3t)) + Ce^{-0.1t},$$


and using the initial condition $I(0) = 0$ we obtain

$$C = -\frac{40}{901},$$

hence

$$I(t) = \frac{4}{901} (10 \cos(3t) + 300 \sin(3t)) - \frac{40}{901} e^{-0.1t}.$$

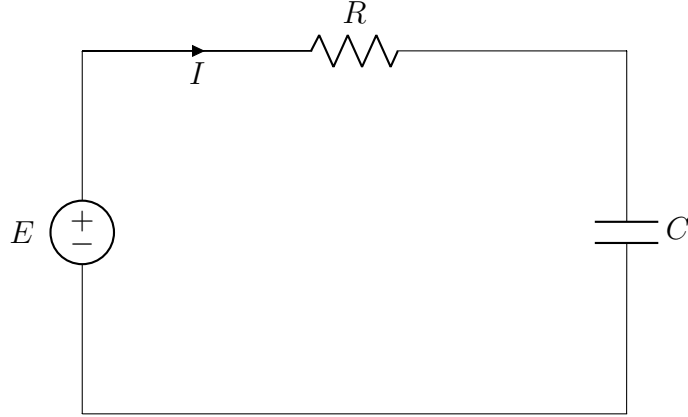- **Exercise #15, page 131.** A resistor (20Ω) and capacitor ($1F$) are linked in series with an electromotive force (emf) $E = E(t)$ in RC circuit.



If the emf is given as $E(t) = 10e^{-0.05t}$ and the current is zero at time $t = 0$, find the maximum charge on the capacitor and the time that it will occur.

Solution: $R = 20\Omega, C = 1F, Q(0) = 0$,

$$E = E_R + E_C \equiv RI + \frac{1}{C}Q = RQ' + \frac{1}{C}Q,$$

$$10e^{-\frac{t}{100}} = 20Q' + Q, \quad Q' = -\frac{1}{20}Q + \frac{1}{2}e^{-\frac{t}{100}}$$

and using as integrating factor $u(t) = e^{\frac{t}{20}}$ we obtain

$$(e^{\frac{t}{20}}Q) = \frac{1}{2}e^{\frac{t}{25}},$$

$$e^{\frac{t}{20}}Q(t) = \frac{25}{2}e^{\frac{t}{25}} + C,$$

$$Q(t) = 12.5e^{\frac{t}{25} - \frac{t}{20}} + Ce^{-\frac{t}{20}} \equiv 12.5e^{-0.01t} + Ce^{-\frac{t}{20}}.$$

Using the initial condition $Q(0) = 0 \equiv 12.5 + C$ we obtain $C = -12.5$, and therefore

$$Q(t) = 12.5e^{-0.01t}(e^{-0.04t} - 1).$$

To find the maximum charge, we compute

$$Q'(t) = e^{-0.05t}(625 \times 10^{-4} - 125 \times 10^{-4}e^{0.04t}),$$

hence the maximum charge is when $Q'(T) = 0$, i.e.,

$$T = 25 \ln(5),$$

$$Q(25 \ln(5)) \approx 6.6874.$$